

# 3810: Computer Organization

## Lecture 3: Basic MIPS Architecture

Anton Burtsev  
October, 2022


# Basic MIPS Architecture

- Now that we understand clocks and storage of states,
- we'll design a simple CPU that executes:
  - basic math (add, sub, and, or, slt)
  - memory access (lw and sw)
  - branch and jump instructions (beq and j)

# Implementation Overview

- We need memory
  - to store instructions
  - to store data
  - for now, let's make them separate units
- We need registers, ALU, and a whole lot of control logic
- CPU operations common to all instructions:
  - use the program counter (PC) to pull instruction out of instruction memory
  - read register values

# View from 30,000 Feet

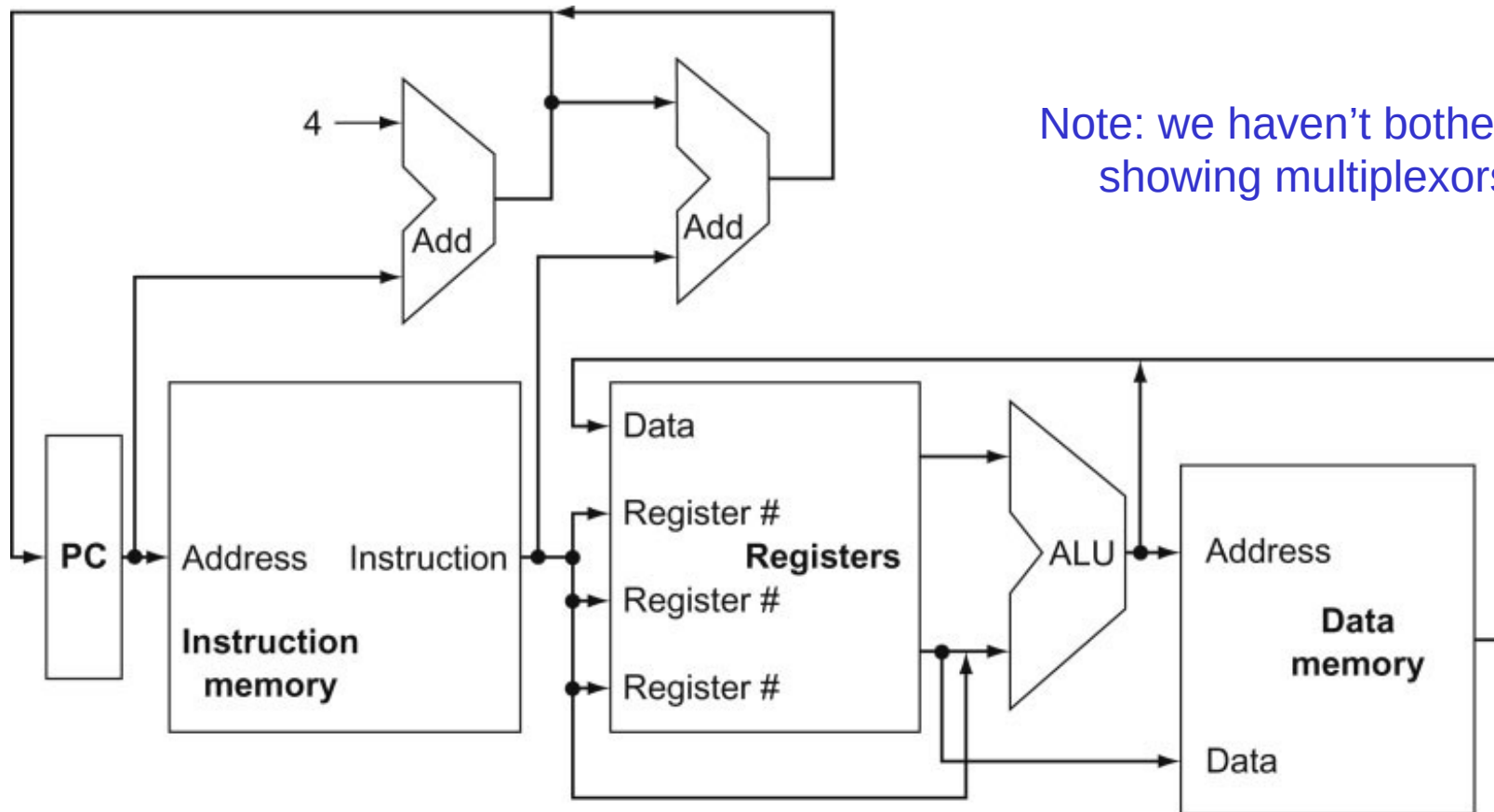

Note: we haven't bothered showing multiplexors

- What is the role of the Add units?
- Explain the inputs to the data memory unit
- Explain the inputs to the ALU
- Explain the inputs to the register unit


Source: H&P textbook

# Implementing R-type Instructions

- Instructions of the form `add $r1, $r2, $r3`
- Explain the role of each signal



a. Registers

 


b. ALU

Source: H&P textbook

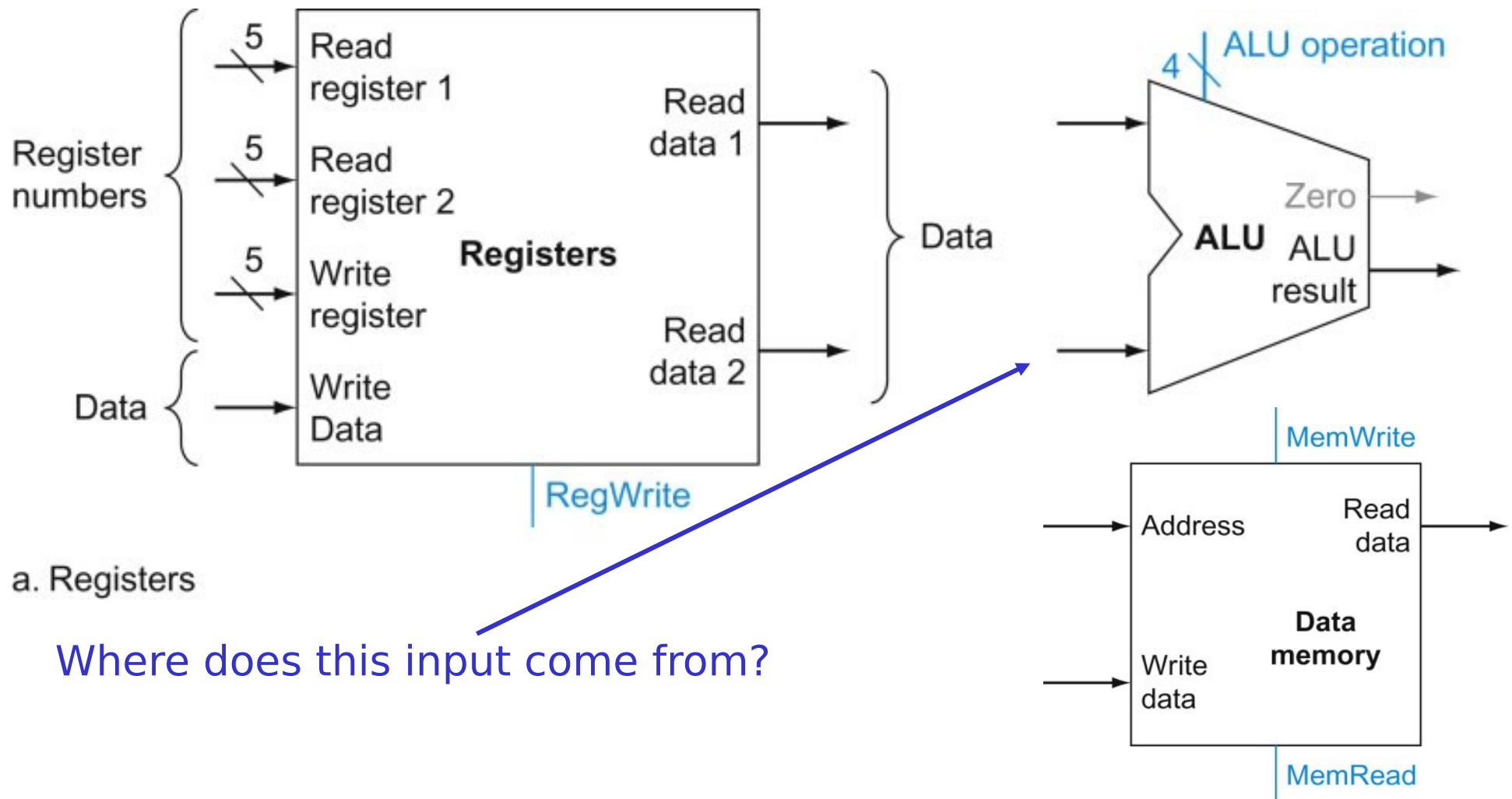
# Implementing Loads/Stores

- Instructions of the form `lw $r1, 8($r2)` and `sw $r1, 8($r2)`
- Explain the role of each signal



 
# Implementing J-type Instructions

- Instructions of the form `beq $r1, $r2, offset`




Source: H&P textbook

# View from 10,000 Feet

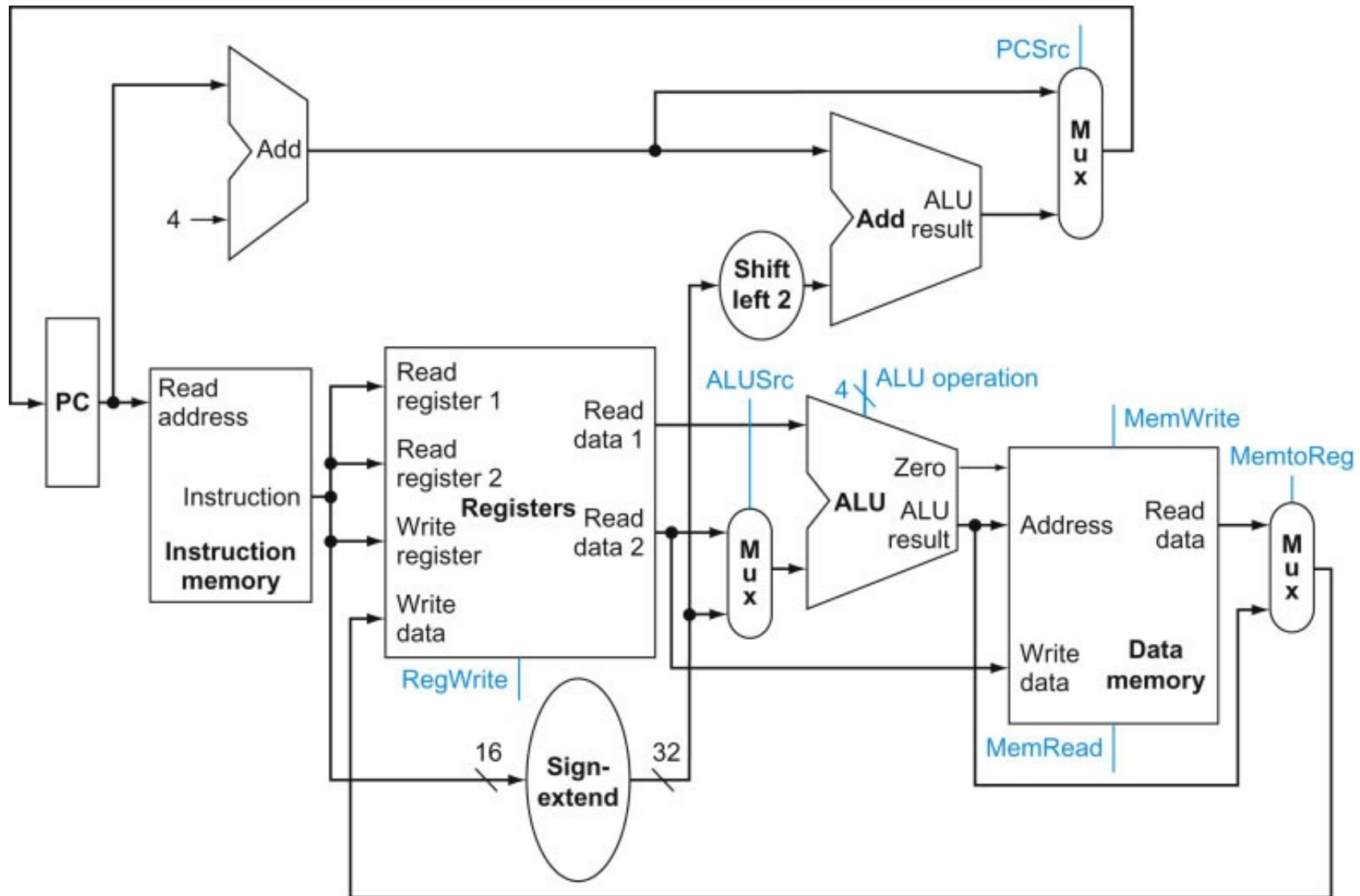




# View from 5,000 Feet

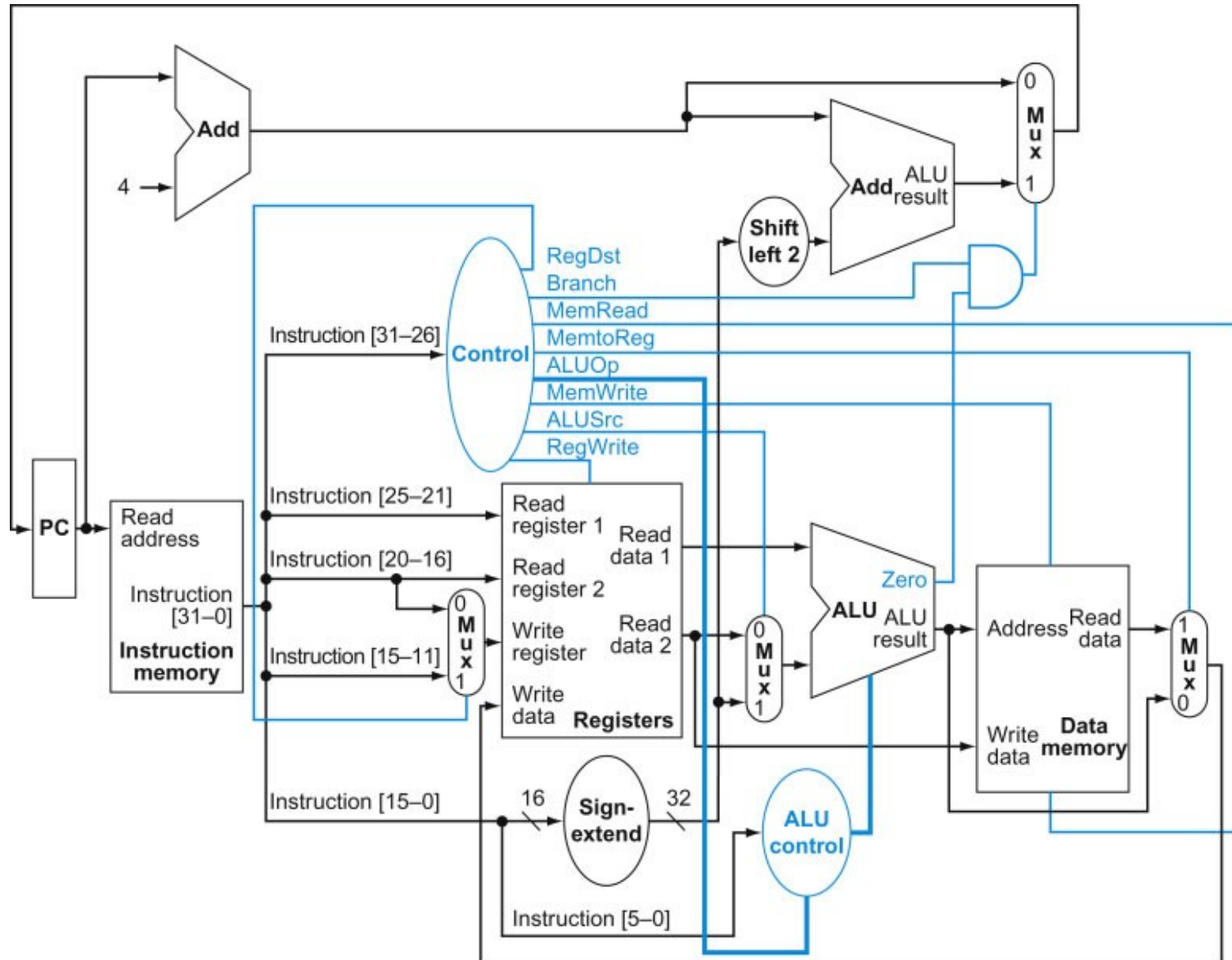

Thank you!

# Clocking Methodology

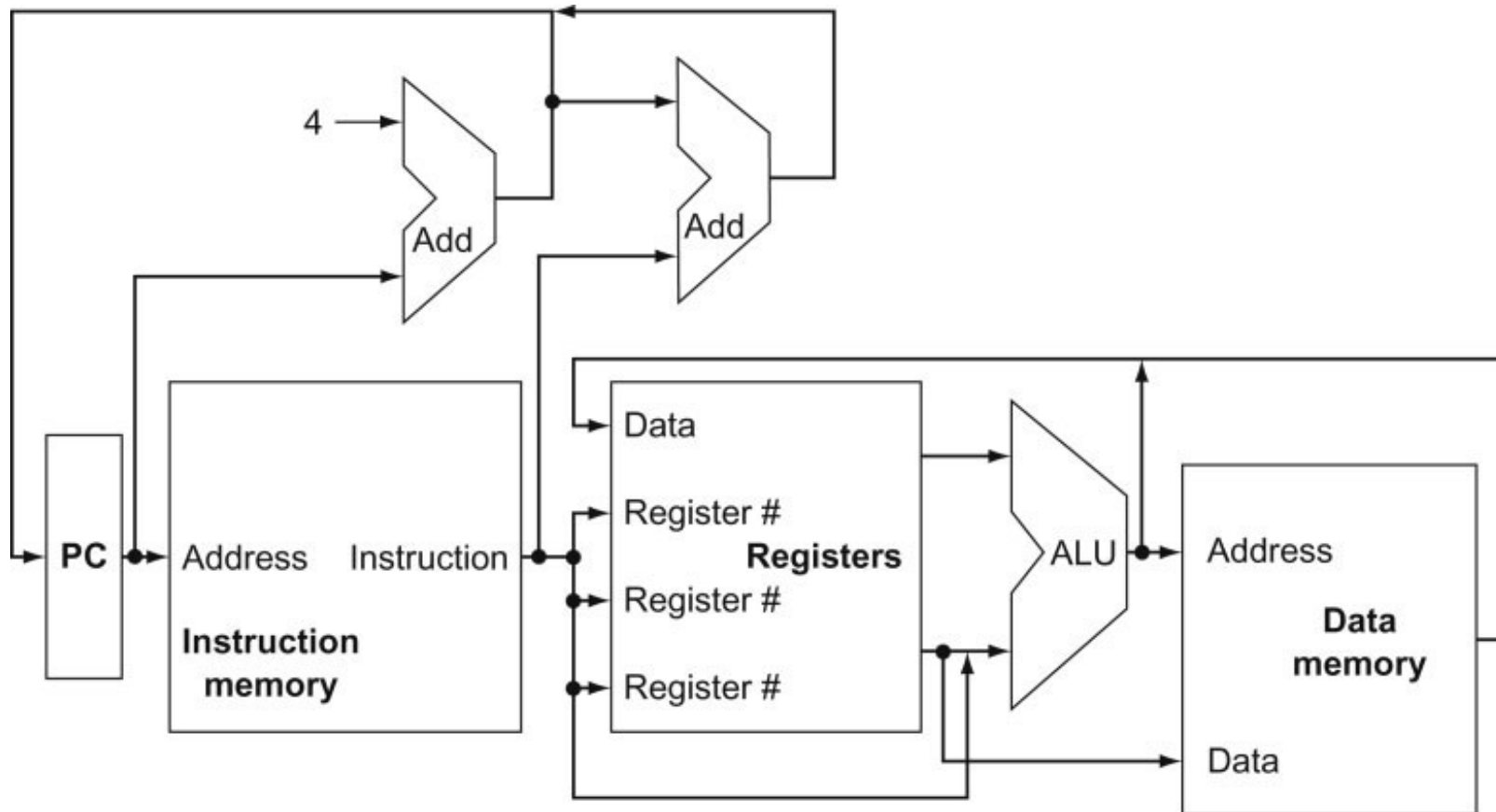

Source: H&P textbook

- Which of the above units need a clock?
- What is being saved (latched) on the rising edge of the clock?
- Keep in mind that the latched value remains there for an entire cycle