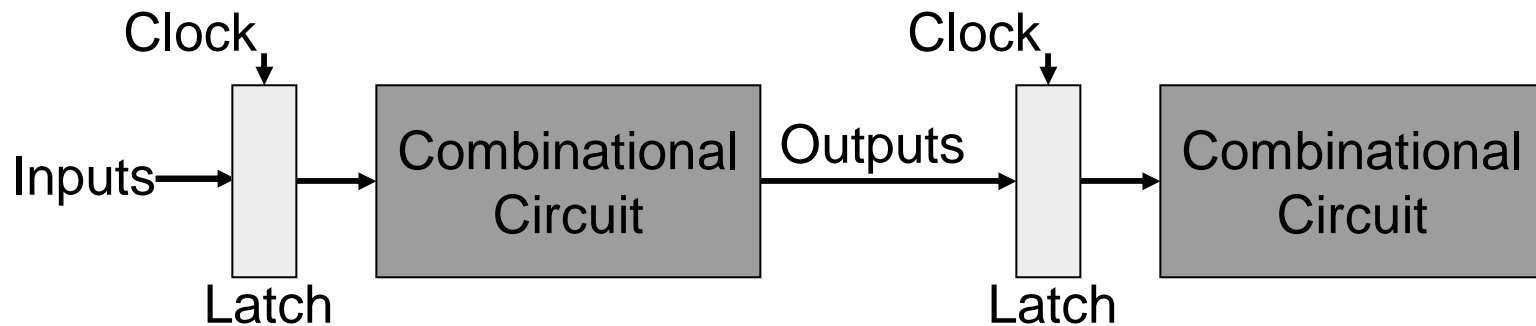


Lecture 14: FSM and Basic CPU Design

- Today's topics:
 - Finite state machines
 - Single-cycle CPU
- Reminder: midterm on Tue 10/24
 - will cover Chapters 1-4, App A, B
 - shorter than last year
 - if you understand all slides, assignments, you will ace 90% of the test


Sequential Circuits

- We want the clock to act like a start and stop signal – a “latch” is a storage device that stores its inputs at a rising clock edge and this storage will not change until the next rising clock edge




Finite State Machine

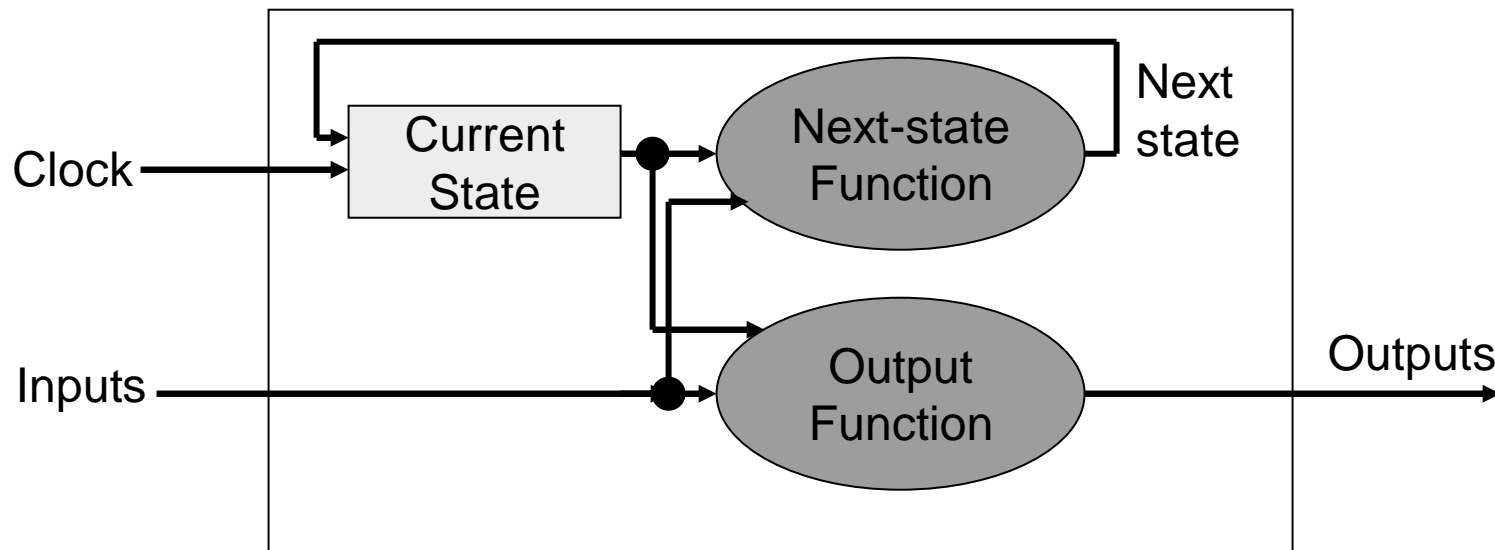- A sequential circuit is described by a variation of a truth table – a finite state diagram (hence, the circuit is also called a finite state machine)
- Note that state is updated only on a clock edge



State Diagrams

 - Each state is shown with a circle, labeled with the state value – the contents of the circle are the outputs
- An arc represents a transition to a different state, with the inputs indicated on the label



This is a state diagram for ____?

3-Bit Counter

- Consider a circuit that stores a number and increments the value on every clock edge – on reaching the largest value, it starts again from 0

Draw the state diagram:


- How many states?
- How many inputs?

3-Bit Counter

- Consider a circuit that stores a number and increments the value on every clock edge – on reaching the largest value, it starts again from 0

Draw the state diagram:

- How many states?
- How many inputs?

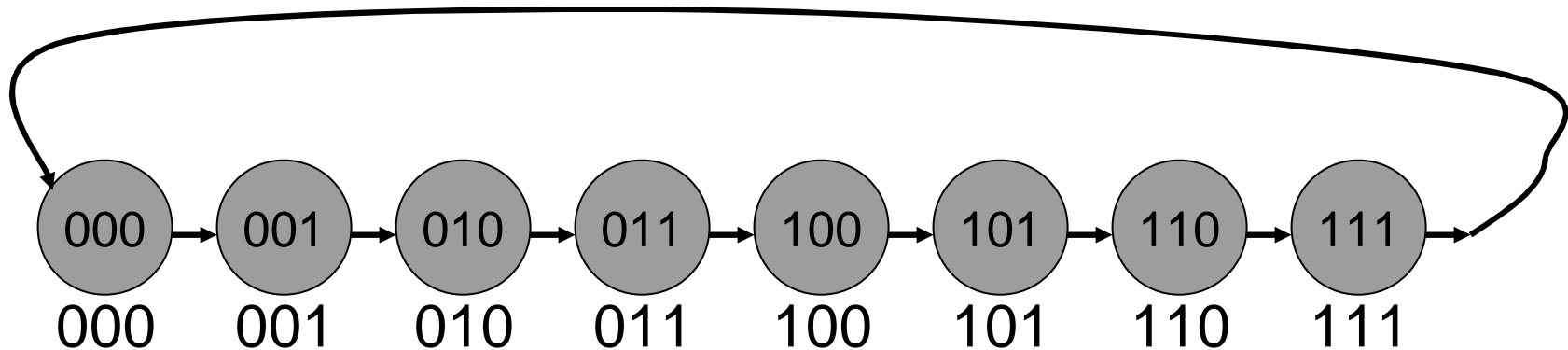

Traffic Light Controller

- Problem description: A traffic light with only green and red; either the North-South road has green or the East-West road has green (both can't be red); there are detectors on the roads to indicate if a car is on the road; the lights are updated every 30 seconds; a light need change only if a car is waiting on the other road

State Transition Table:

How many states?

How many inputs?

How many outputs?

State Transition Table

- Problem description: A traffic light with only green and red; either the North-South road has green or the East-West road has green (both can't be red); there are detectors on the roads to indicate if a car is on the road; the lights are updated every 30 seconds; a light must change only if a car is waiting on the other road


State Transition Table:

CurrState	InputEW	InputNS	NextState=Output
N	0	0	N
N	0	1	N
N	1	0	E
N	1	1	E
E	0	0	E
E	0	1	N
E	1	0	E
E	1	1	N

State Diagram

State Transition Table:

CurrState	InputEW	InputNS	NextState=Output
N	0	0	N
N	0	1	N
N	1	0	E
N	1	1	E
E	0	0	E
E	0	1	N
E	1	0	E
E	1	1	N

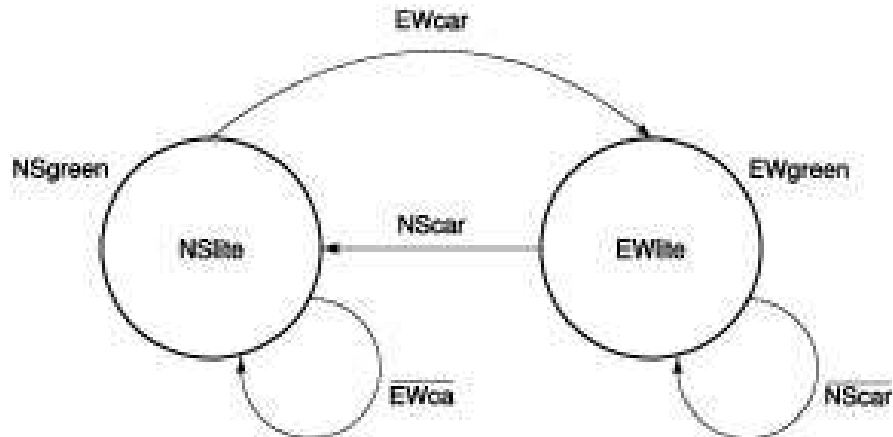


Basic MIPS Architecture

- Now that we understand clocks and storage of states, we'll design a simple CPU that executes:
 - basic math (add, sub, and, or, slt)
 - memory access (lw and sw)
 - branch and jump instructions (beq and j)

Implementation Overview

- We need memory
 - to store instructions
 - to store data
 - for now, let's make them separate units
- We need registers, ALU, and a whole lot of control logic
- CPU operations common to all instructions:
 - use the program counter (PC) to pull instruction out of instruction memory
 - read register values


View from 30,000 Feet

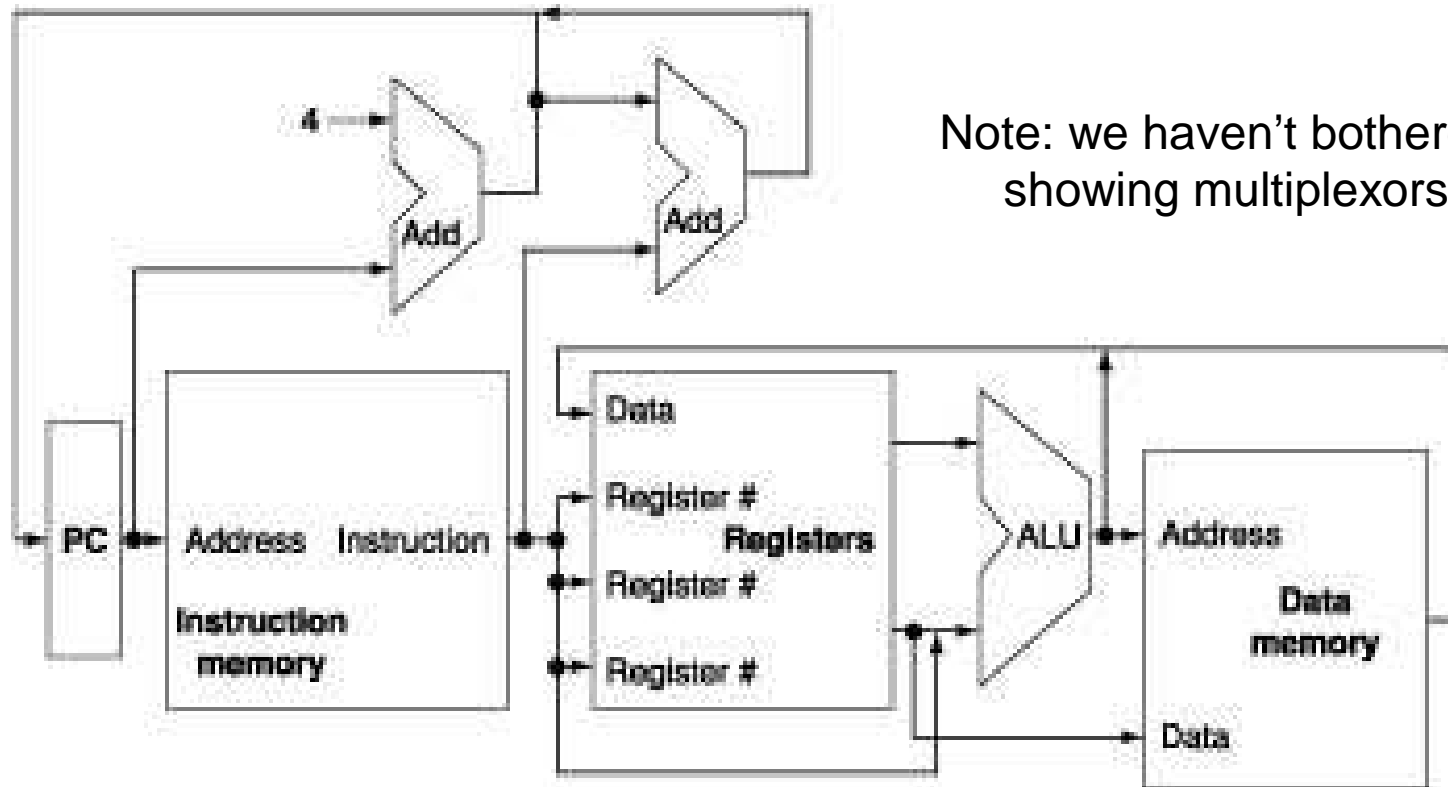

Note: we haven't bothered showing multiplexors

- What is the role of the Add units?
- Explain the inputs to the data memory unit
- Explain the inputs to the ALU
- Explain the inputs to the register unit


Clocking Methodology

 

- Which of the above units need a clock?
- What is being saved (latched) on the rising edge of the clock?
Keep in mind that the latched value remains there for an entire cycle


Implementing R-type Instructions

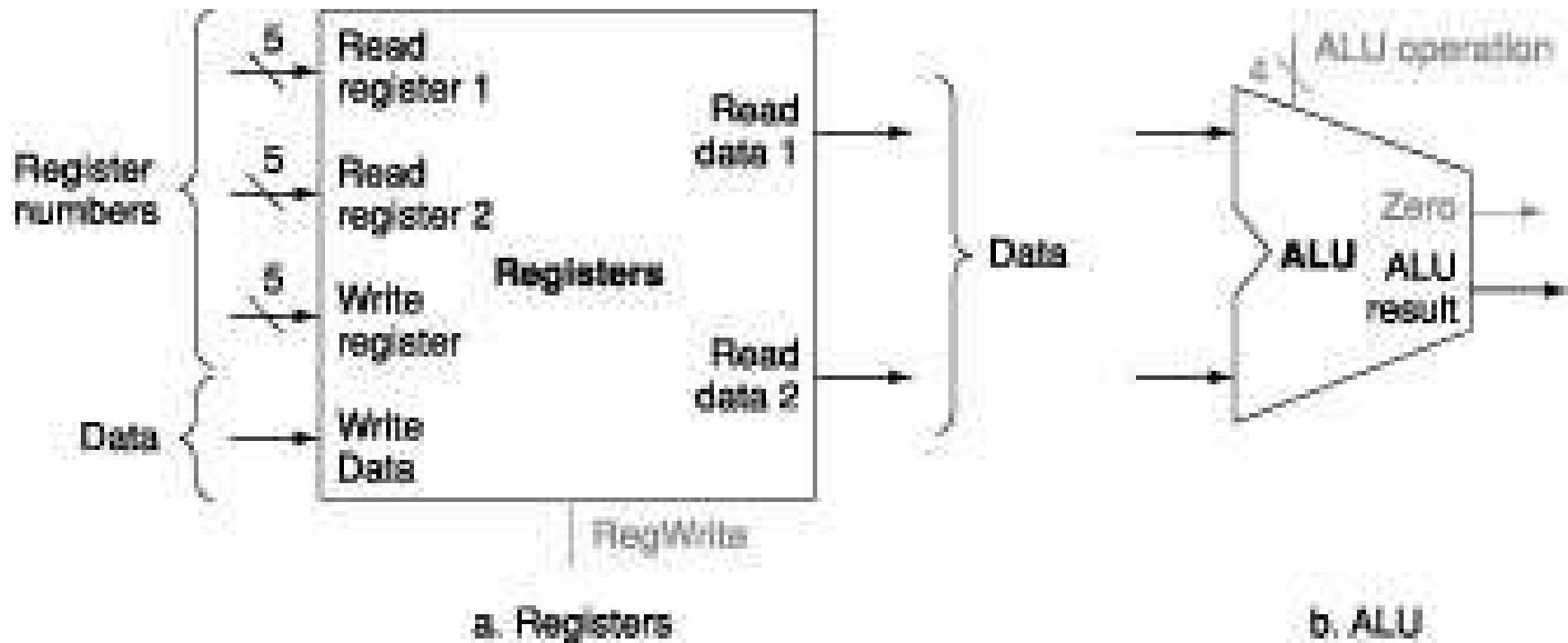- Instructions of the form `add $t1, $t2, $t3`
- Explain the role of each signal




Implementing Loads/Stores

 - Instructions of the form `lw $t1, 8($t2)` and `sw $t1, 8($t2)`




Implementing J-type Instructions

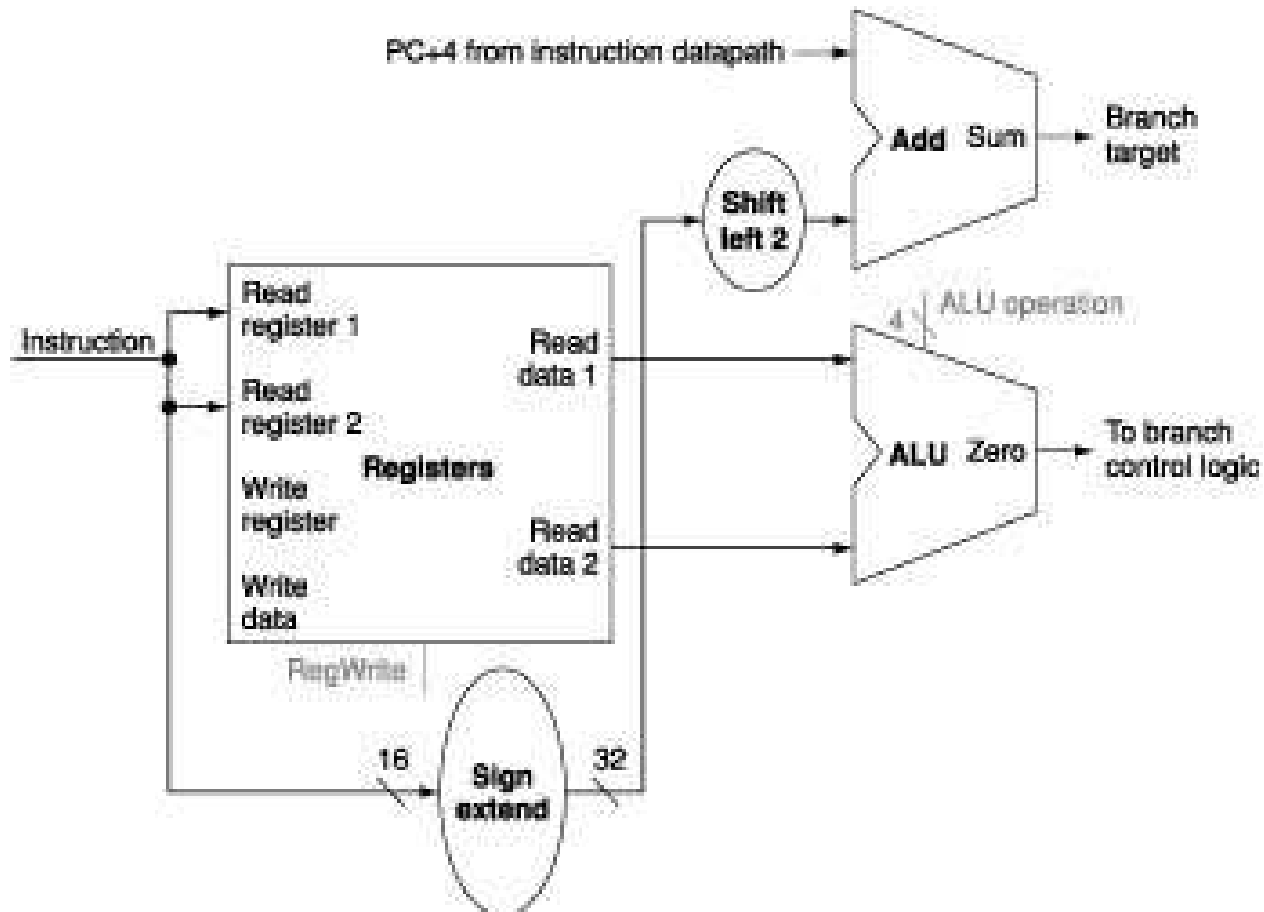- Instructions of the form `beq $t1, $t2, offset`




View from 10,000 Feet

 

Single Vs. Multi-Cycle Machine

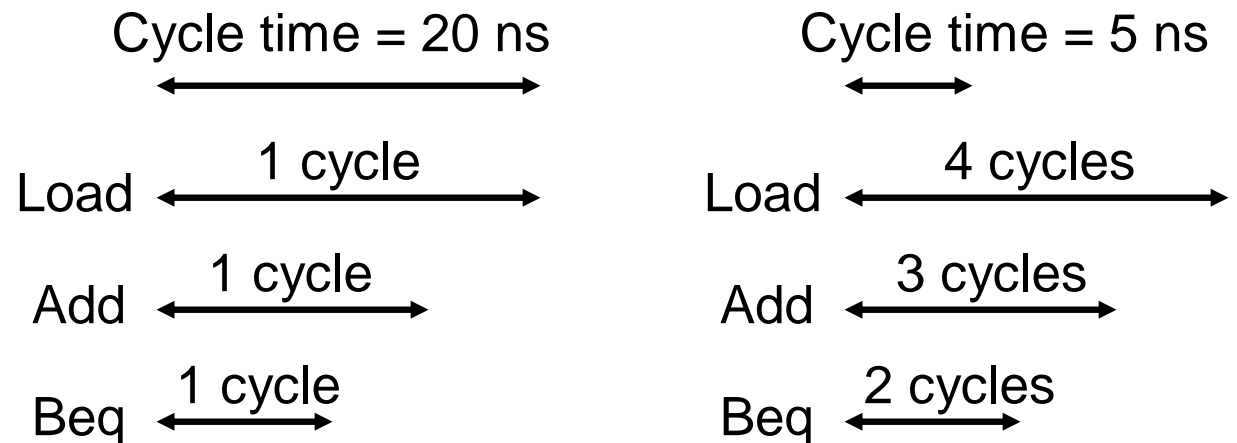- In this implementation, every instruction requires one cycle to complete → cycle time = time taken for the slowest instruction
- If the execution was broken into multiple (faster) cycles, the shorter instructions can finish sooner



Time for a load, add, and beq = 60 ns

45 ns

Title

- Bullet