

# Lecture 16: Basic CPU Design

---

- Today's topics:
  - Single-cycle CPU
  - Multi-cycle CPU
- Reminder:
  - Assignment 6 will be posted today – due in a week

# Basic MIPS Architecture

---

- Now that we understand clocks and storage of states, we'll design a simple CPU that executes:
  - basic math (add, sub, and, or, slt)
  - memory access (lw and sw)
  - branch and jump instructions (beq and j)


# Implementation Overview

---

- We need memory
  - to store instructions
  - to store data
  - for now, let's make them separate units
- We need registers, ALU, and a whole lot of control logic
- CPU operations common to all instructions:
  - use the program counter (PC) to pull instruction out of instruction memory
  - read register values

# View from 30,000 Feet

---

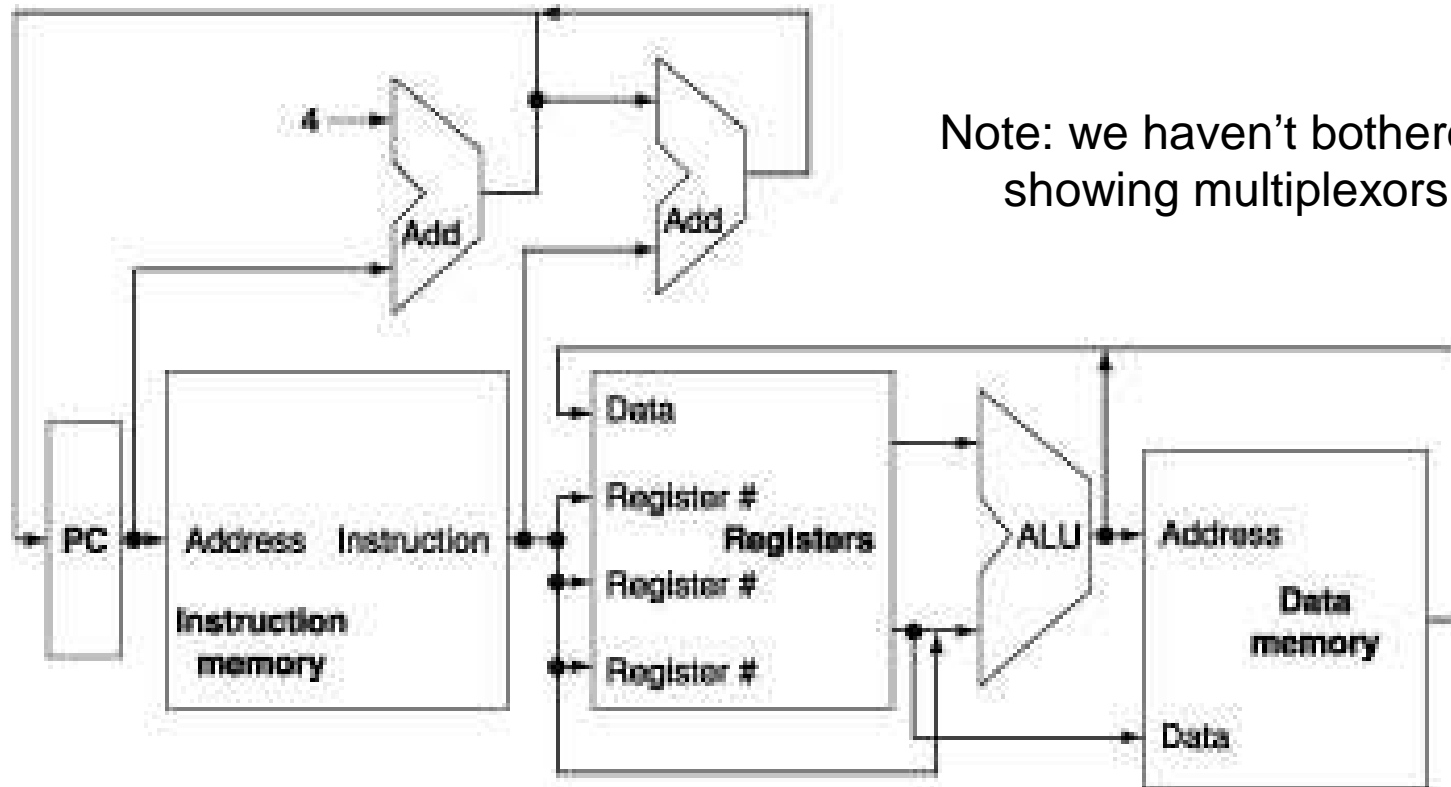


Note: we haven't bothered showing multiplexors

- What is the role of the Add units?
- Explain the inputs to the data memory unit
- Explain the inputs to the ALU
- Explain the inputs to the register unit

# Clocking Methodology


---

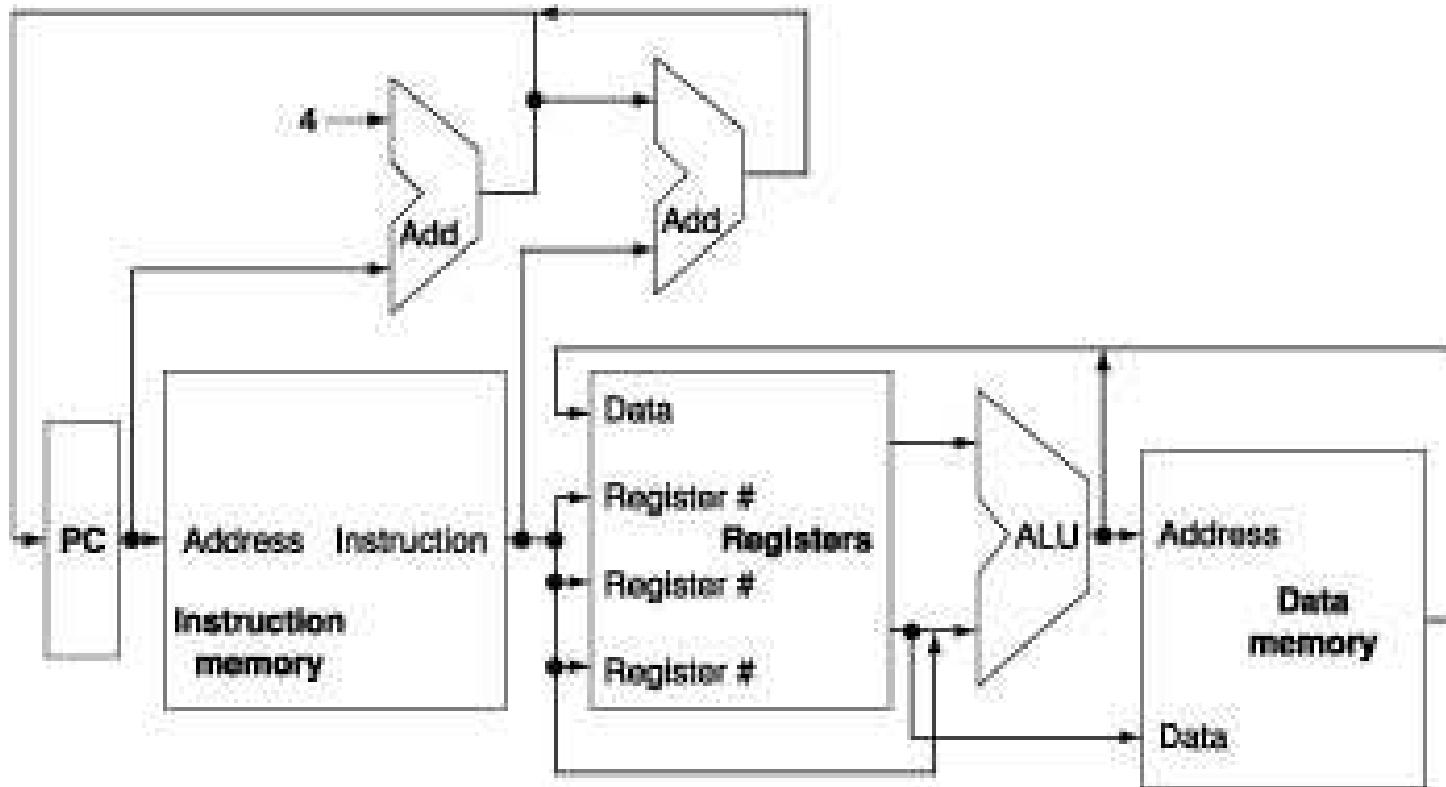

- Which of the above units need a clock?
- What is being saved (latched) on the rising edge of the clock?  
Keep in mind that the latched value remains there for an entire cycle

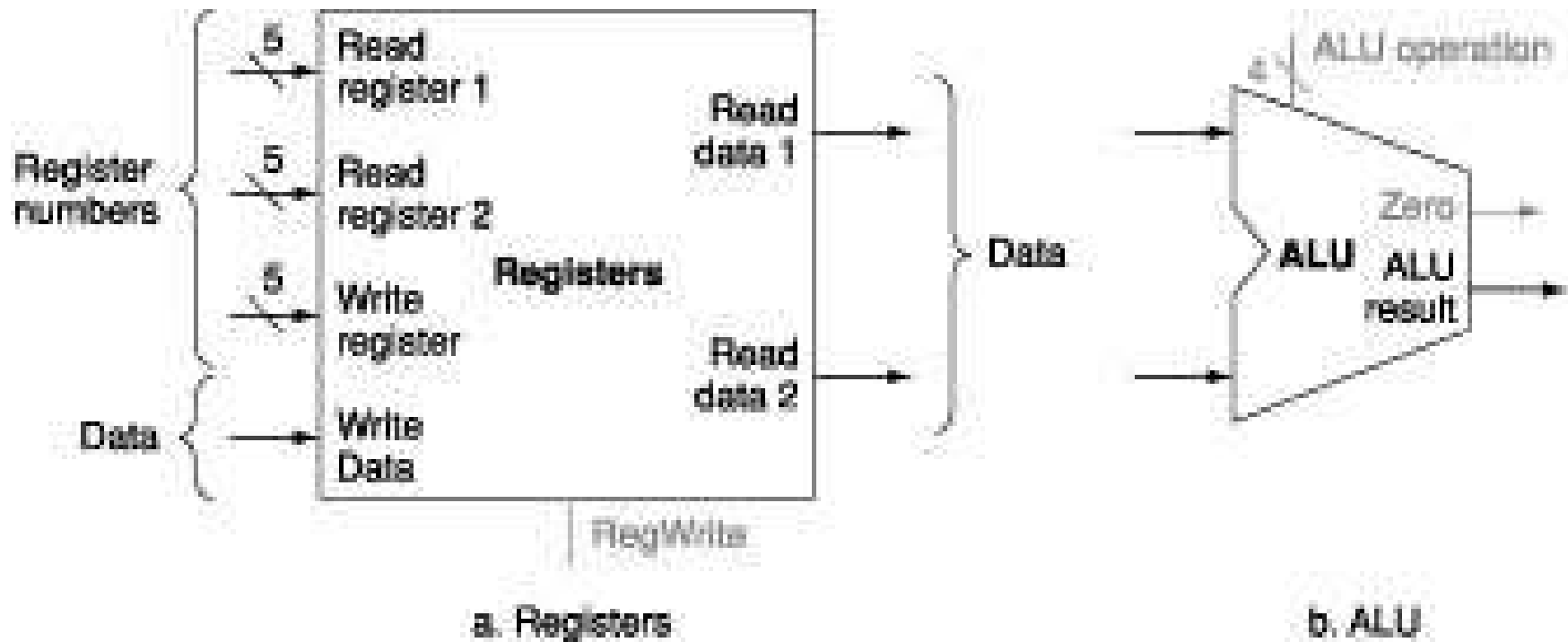
# Implementing R-type Instructions

- Instructions of the form `add $t1, $t2, $t3`
- Explain the role of each signal



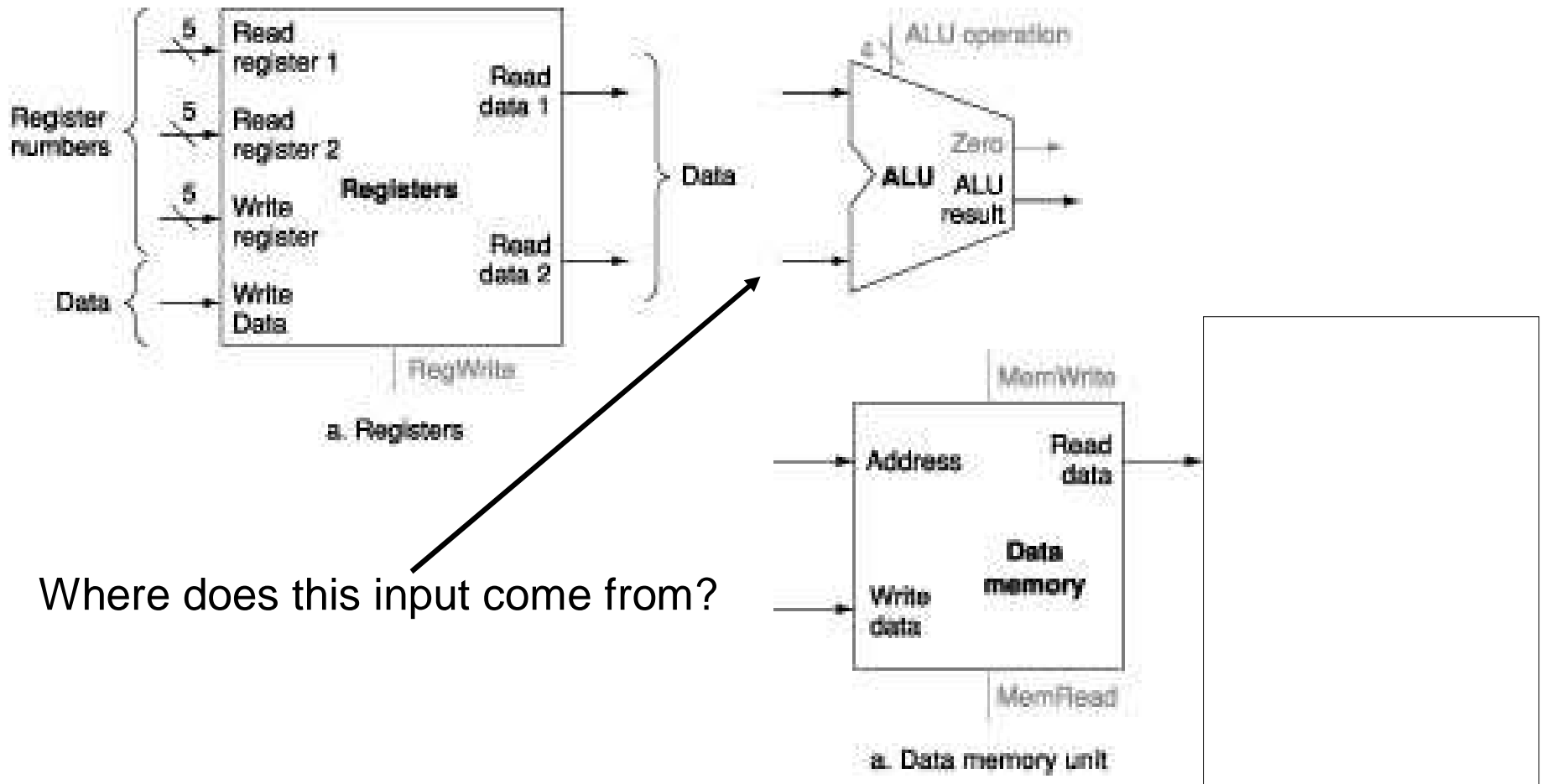
# Implementing Loads/Stores

- Instructions of the form `lw $t1, 8($t2)` and `sw $t1, 8($t2)`



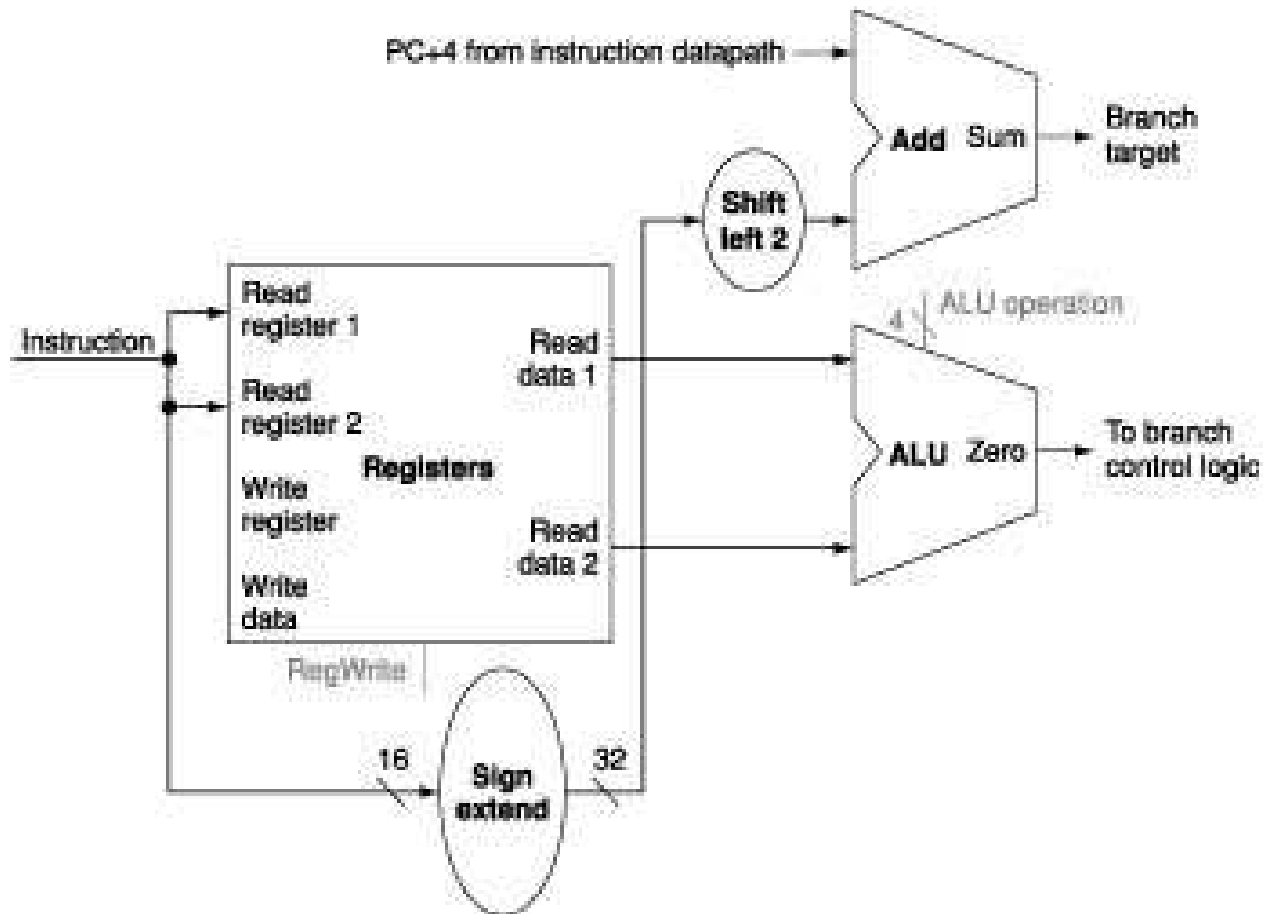
# Implementing J-type Instructions

- Instructions of the form `beq $t1, $t2, offset`






# View from 10,000 Feet

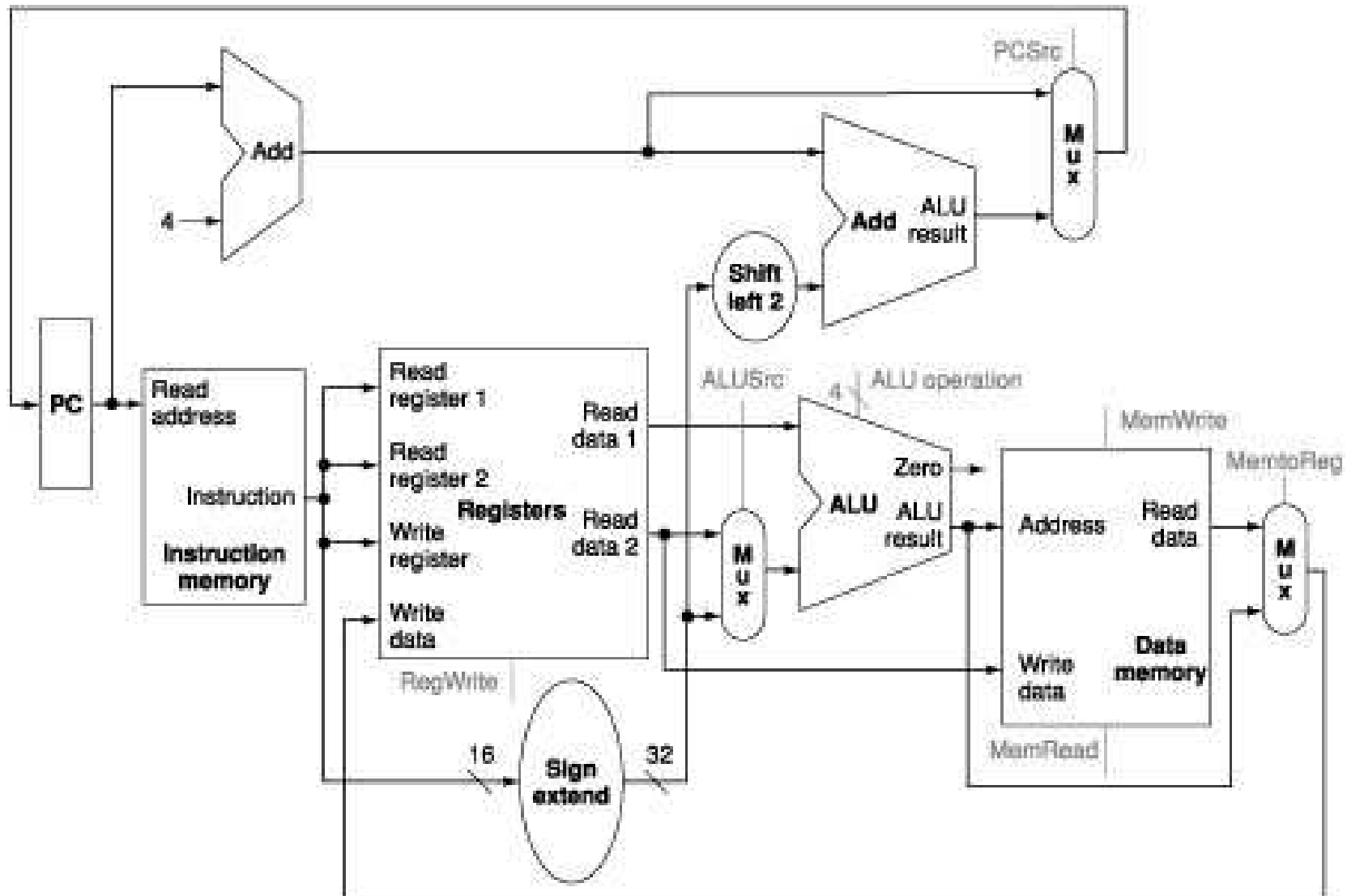


# View from 5,000 Feet

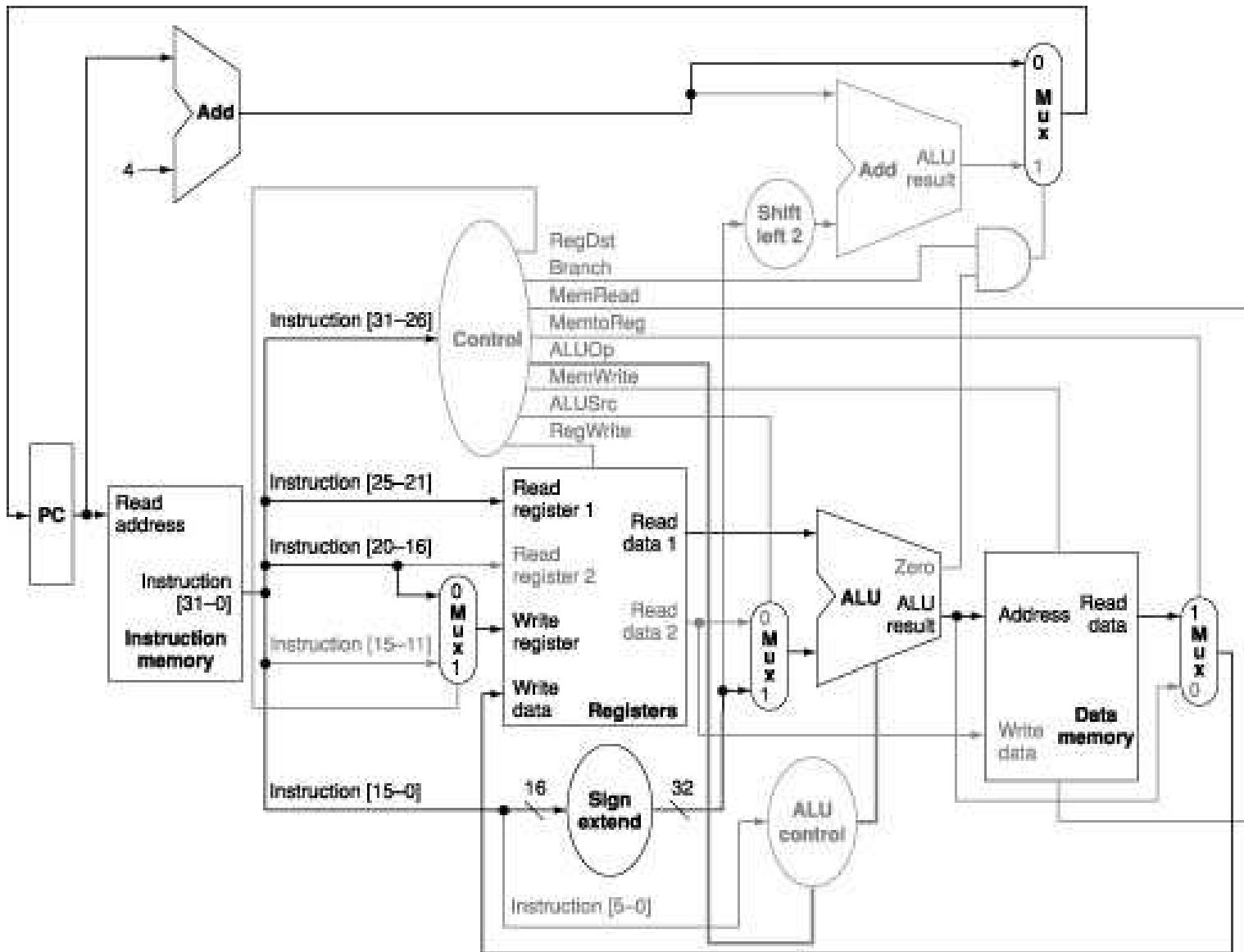
 
# Single Vs. Multi-Cycle Machine

---

- In this implementation, every instruction requires one cycle to complete → cycle time = time taken for the slowest instruction
- If the execution was broken into multiple (faster) cycles, the shorter instructions can finish sooner




Time for a load, add, and beq = 60 ns

45 ns

# Multi-Cycle Processor

---

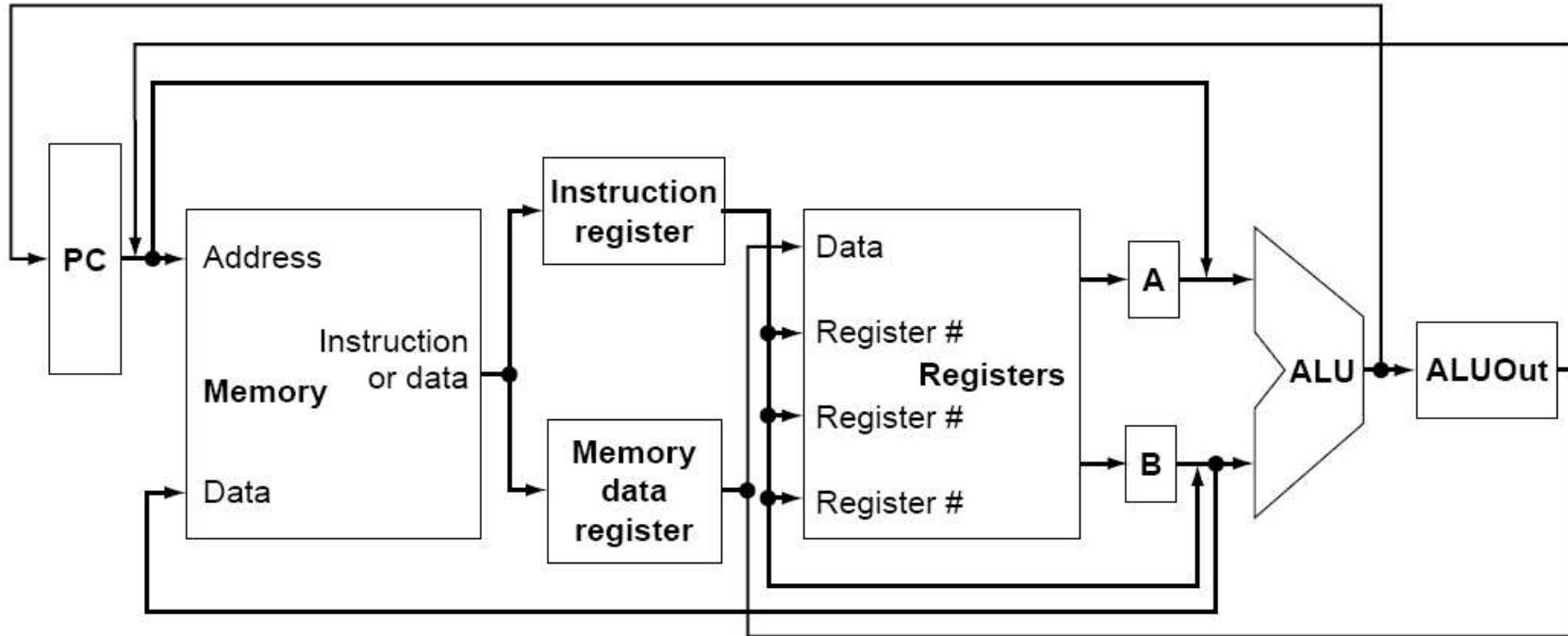

- Single memory unit shared by instructions and memory
- Single ALU also used for PC updates
- Registers (latches) to store the result of every block

# Cycle 1

---

- The PC is used to select the appropriate instruction out of the memory unit
- The instruction is latched into the instruction register at the end of the clock cycle
- The ALU performs  $PC+4$  and stores it in the PC at the end of the clock cycle (note that ALU is free this cycle)
- The control circuits must now be “cycle-aware” – the new PC need not look up the instr-memory until we’re done executing the current instruction

# Cycle 2

---

- The instruction specifies the required register values – these are read from the register file and stored in latches A and B (this happens even if the operands are not required)
- The last 16 bits are also used to compute  $PC+4+offset$  (in case this instruction turns out to be a branch) – this is latched into *ALUOut*
- Note that we haven't yet figured out the instruction type, so the above operations are “speculative”

# Cycle 3

---

The operations depend on the instruction type

- Memory access: the address is computed by adding the offset to the value read from the register file, result is latched into ALUOut
- ALU: ALU operations are performed on the values read from the register file and the result is latched into ALUOut
- Branch: the ALU performs the operations for “beq” and if the branch happens, the branch target (currently in ALUOut) is latched into the PC at the end of the cycle
- Note that the branch operation has completed by the end of cycle 3, the other two are still

# Cycle 4

---

- Memory access: the address in ALUOut is used to pick out a word from memory – this is latched into the memory data register
- ALU: the result latched into ALUOut is fed as input to the register file, the instruction stored in the instruction-latch specifies where the result is written into
- At the end of this cycle, the ALU operation and memory writes are complete



# Cycle 5

---

- Memory read: the value read from memory (and latched in the memory data register) is now written into the register file
- Summary:
  - Branches and jumps: 3 cycles
  - ALU, stores: 4 cycles
  - Memory access: 5 cycles

ALU is slower since it requires a register file write  
Store is slower since it requires a data memory write  
Load is slower since it requires a data memory read  
and a register file write

# Average CPI

---

- Now we can compute average CPI for a program: if the given program is composed of loads (25%), stores (10%), branches (13%), and ALU ops (52%), the average CPI is

$$0.25 \times 5 + 0.1 \times 4 + 0.13 \times 3 + 0.52 \times 4 = 4.12$$


- You can break this CPU design into shorter cycles, for example, a load would then take 10 cycles, stores 8, ALU 8, branch 6 → average CPI would double, but so would the clock speed, the net performance would remain roughly the same

Later, we'll see that this strategy does help in most other cases.
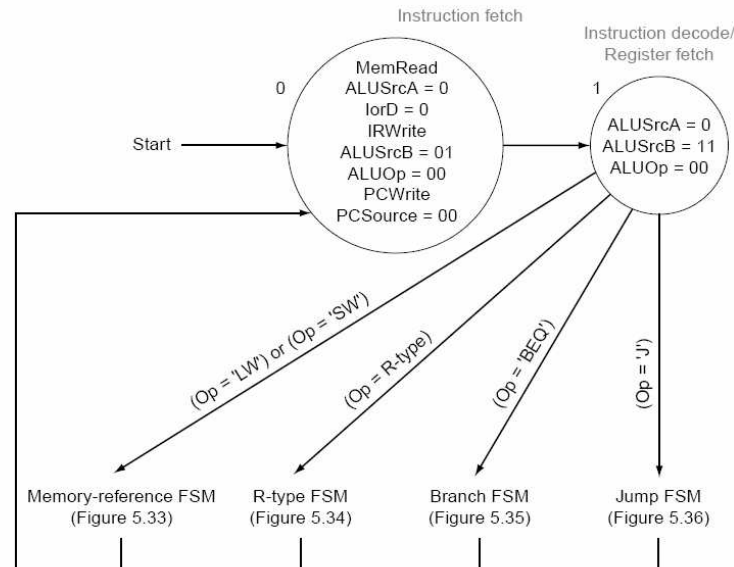
# Control Logic

- Note that the control signals for every unit are determined by two factors:
  - the instruction type
  - the cycle number for this instruction

The control is therefore implemented as a finite state machine – every cycle, the FSM transitions to a new state with a certain set of outputs (the control signals) and this is a function of the inputs (the instr type)



# Title

---

- Bullet