

# Lecture 13: Sequential Circuits, FSM

---

- Today's topics:
  - Sequential circuits
  - Finite state machines

# Clocks


---

- A microprocessor is composed of many different circuits that are operating simultaneously – if each circuit  $X$  takes in inputs at time  $TI_X$ , takes time  $TE_X$  to execute the logic, and produces outputs at time  $TO_X$ , imagine the complications in co-ordinating the tasks of every circuit
- A major school of thought (used in most processors built today): all circuits on the chip share a clock signal (a square wave) that tells every circuit when to accept inputs, how much time they have to execute the logic, and when they must produce outputs



# Clock Terminology

---

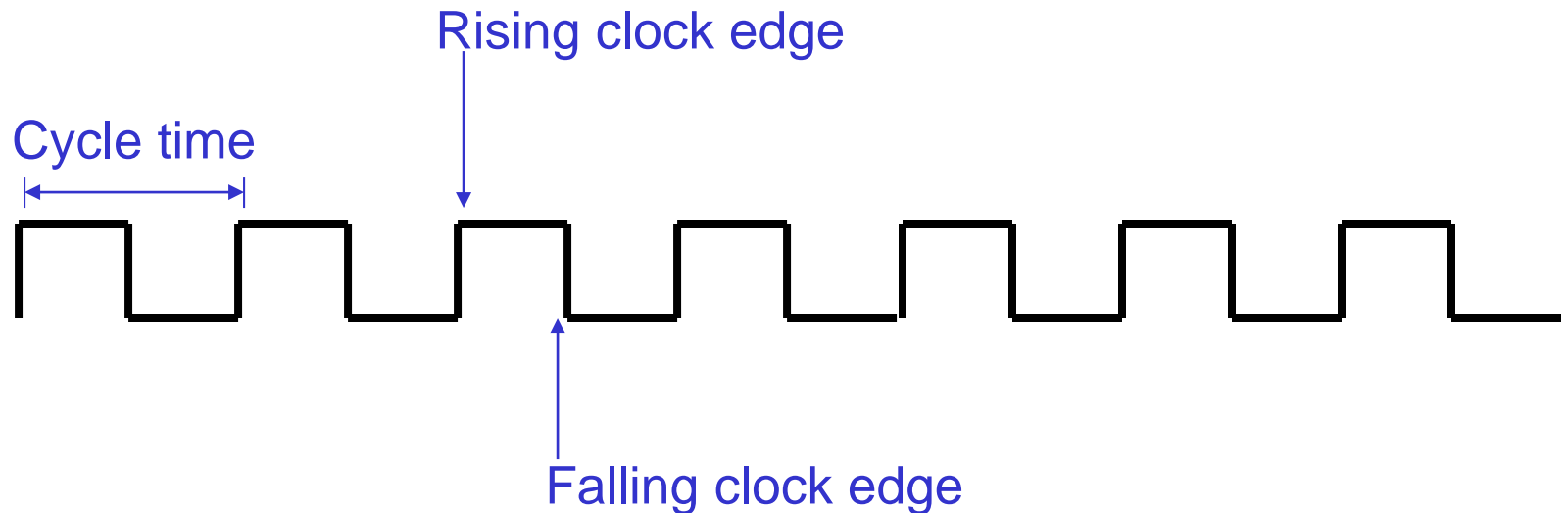


$$4 \text{ GHz} = \text{clock speed} = \frac{1}{\text{cycle time}} = \frac{1}{250 \text{ ps}}.$$

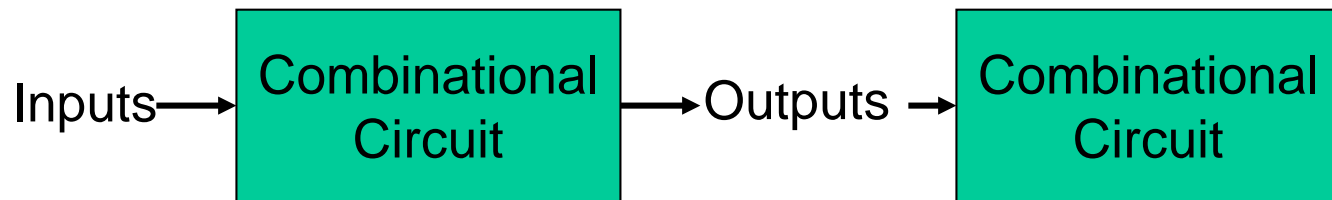
# Sequential Circuits

---

- Until now, circuits were combinational – when inputs change, the outputs change after a while (time = logic delay thru circuit)



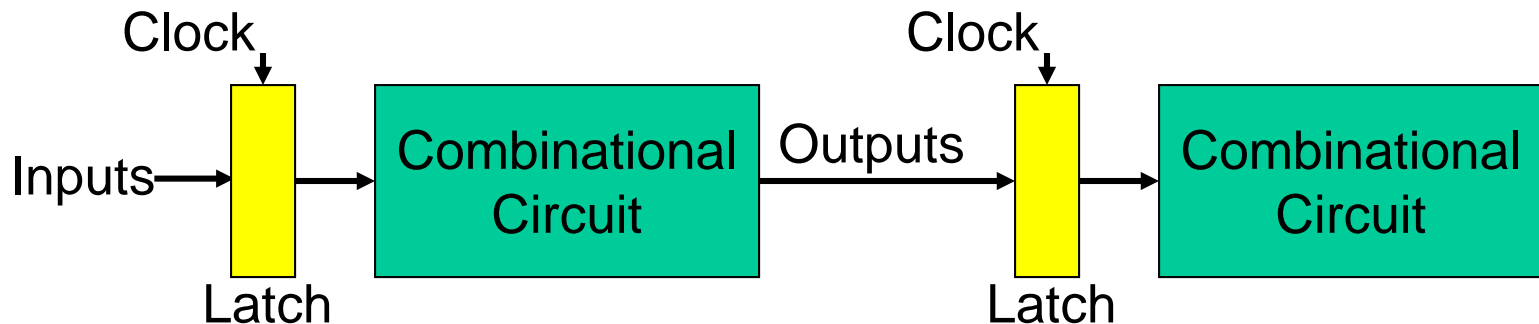
- We want the clock to act like a start and stop signal – a “latch” is a storage device that separates these circuits – it ensures that the inputs to the circuit do not change during a clock cycle


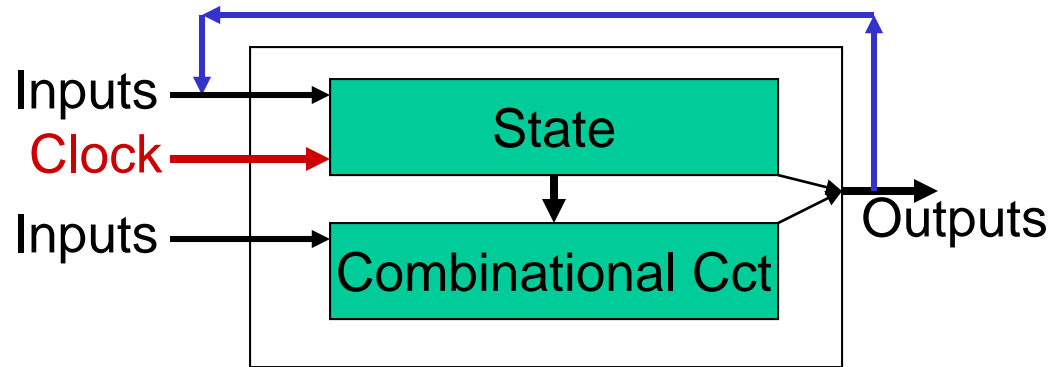
# Sequential Circuits

---

- Sequential circuit: consists of combinational circuit and a storage element
- At the start of the clock cycle, the rising edge causes the “state” storage to store some input values
- This state will not change for an entire cycle (until next rising edge)
- The combinational circuit has some time to accept the value of “state” and “inputs” and produce “outputs”
- Some of the outputs (for example, the value of next “state”) may feed back (but through the latch so they’re only seen in the next cycle)




# Designing a Latch

---

- An S-R latch: set-reset latch
  - When Set is high, a 1 is stored
  - When Reset is high, a 0 is stored
  - When both are low, the previous state is preserved (hence, known as a storage or memory element)
  - Both are high – this set of inputs is not allowed


Verify the above behavior!

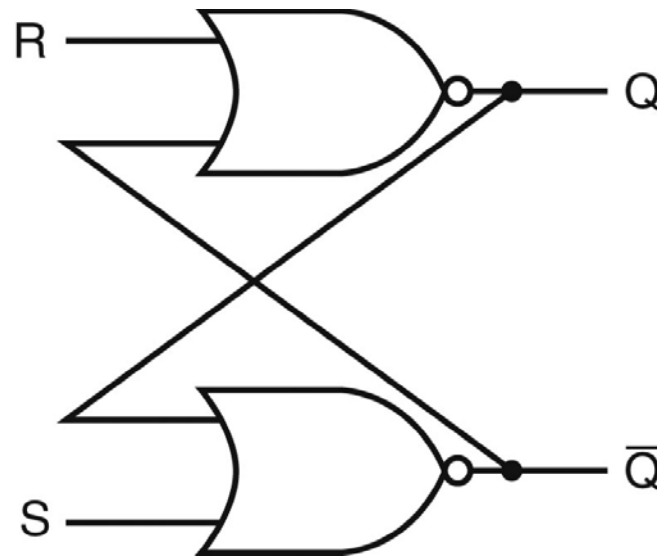
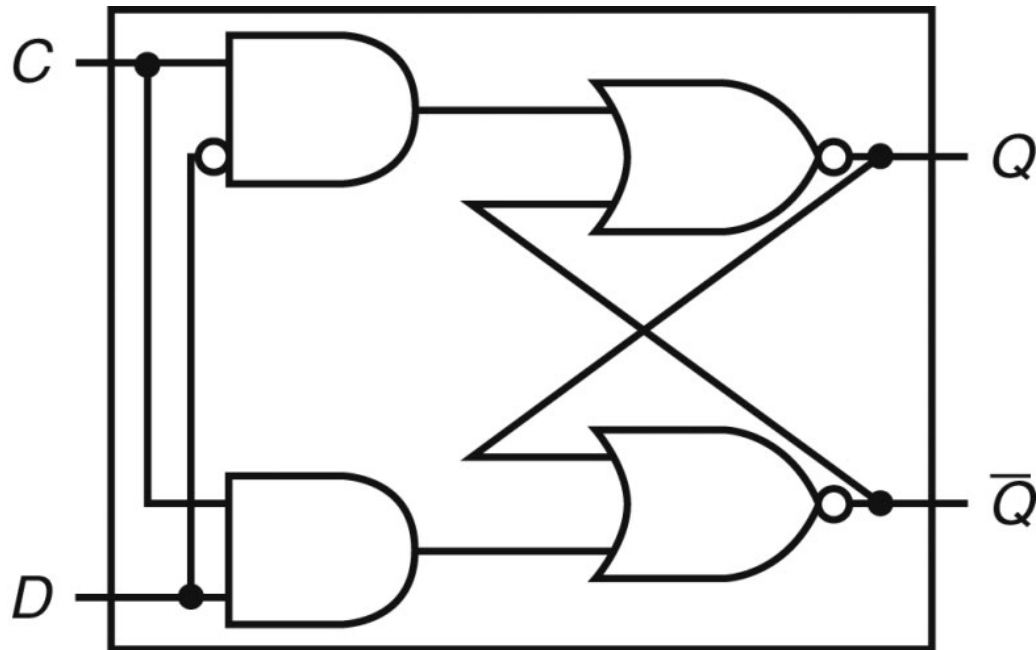
# D Latch

---


- Incorporates a clock
- The value of the input D signal (data) is stored only when the clock is high – the previous state is preserved when the clock is low


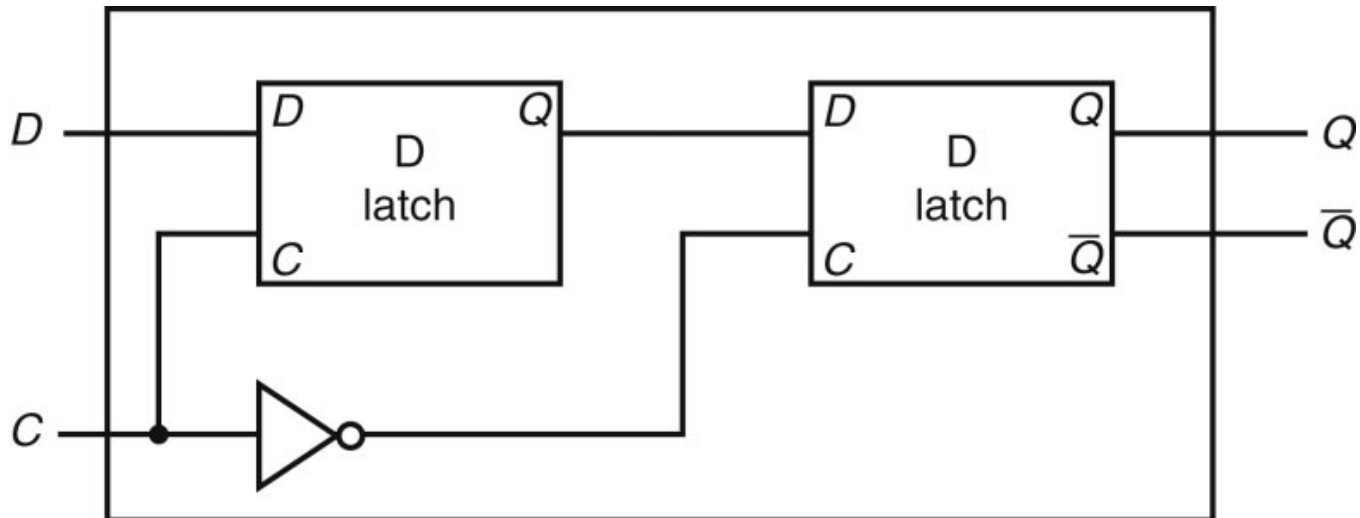
# D Flip Flop

---

- Terminology:  
Latch: outputs can change any time the clock is high (asserted)  
Flip flop: outputs can change only on a clock edge
- Two D latches in series – ensures that a value is stored only on the falling edge of the clock





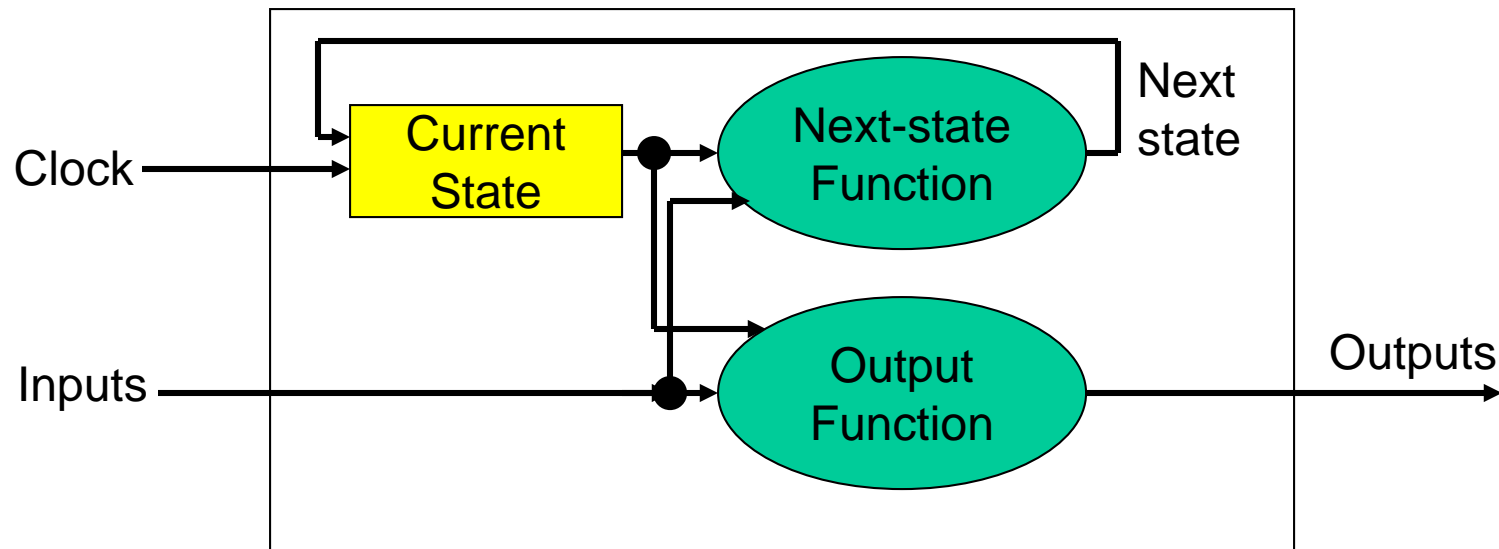
# Finite State Machine

---


- A sequential circuit is described by a variation of a truth table – a finite state diagram (hence, the circuit is also called a finite state machine)
- Note that state is updated only on a clock edge


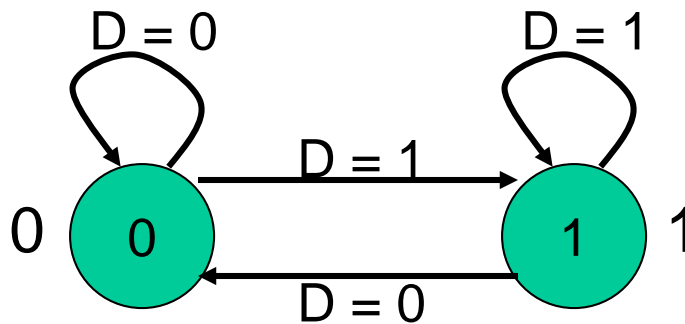
# State Diagrams

---

- Each state is shown with a circle, labeled with the state value – the contents of the circle are the outputs
- An arc represents a transition to a different state, with the inputs indicated on the label



This is a state diagram for \_\_\_\_?

# 3-Bit Counter

---

- Consider a circuit that stores a number and increments the value on every clock edge – on reaching the largest value, it starts again from 0

Draw the state diagram:

- How many states?
- How many inputs?


# 3-Bit Counter

---

- Consider a circuit that stores a number and increments the value on every clock edge – on reaching the largest value, it starts again from 0

Draw the state diagram:

- How many states?
- How many inputs?

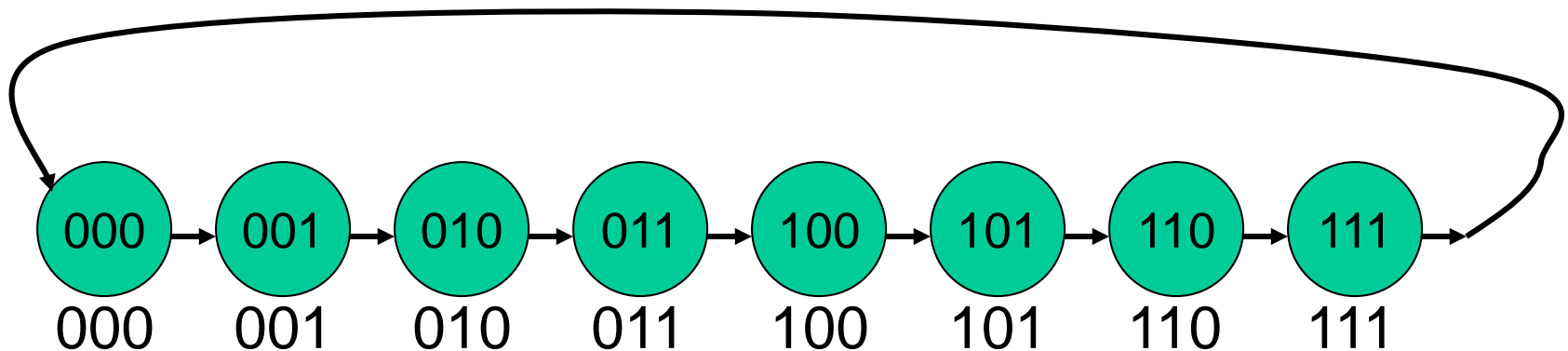

# Traffic Light Controller

---

- Problem description: A traffic light with only green and red; either the North-South road has green or the East-West road has green (both can't be red); there are detectors on the roads to indicate if a car is on the road; the lights are updated every 30 seconds; a light need change only if a car is waiting on the other road

State Transition Table:

How many states?

How many inputs?

How many outputs?

# State Transition Table

---

- Problem description: A traffic light with only green and red; either the North-South road has green or the East-West road has green (both can't be red); there are detectors on the roads to indicate if a car is on the road; the lights are updated every 30 seconds; a light must change only if a car is waiting on the other road


State Transition Table:

CurrState	InputEW	InputNS	NextState=Output
N	0	0	N
N	0	1	N
N	1	0	E
N	1	1	E
E	0	0	E
E	0	1	N
E	1	0	E
E	1	1	N

# State Diagram

State Transition Table:

CurrState	InputEW	InputNS	NextState=Output
N	0	0	N
N	0	1	N
N	1	0	E
N	1	1	E
E	0	0	E
E	0	1	N
E	1	0	E
E	1	1	N

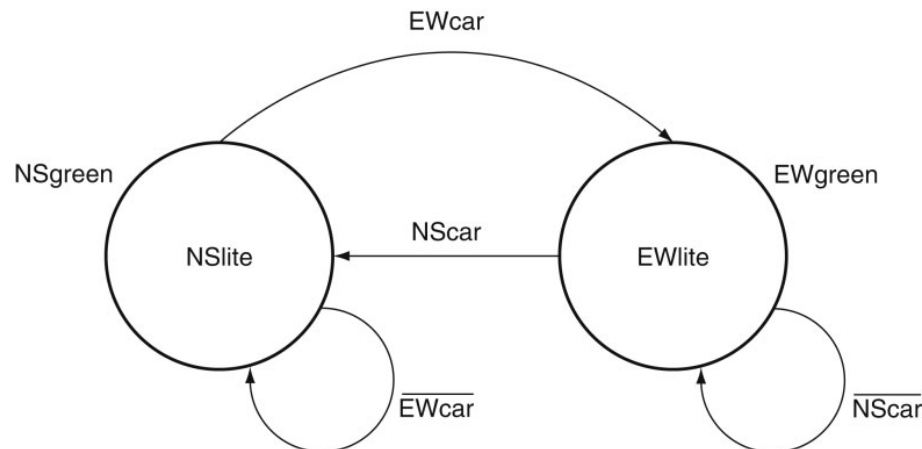

Source: H&P textbook

# Basic MIPS Architecture

---

- Now that we understand clocks and storage of states, we'll design a simple CPU that executes:
  - basic math (add, sub, and, or, slt)
  - memory access (lw and sw)
  - branch and jump instructions (beq and j)




# Implementation Overview

---

- We need memory
  - to store instructions
  - to store data
  - for now, let's make them separate units
- We need registers, ALU, and a whole lot of control logic
- CPU operations common to all instructions:
  - use the program counter (PC) to pull instruction out of instruction memory
  - read register values

# View from 30,000 Feet

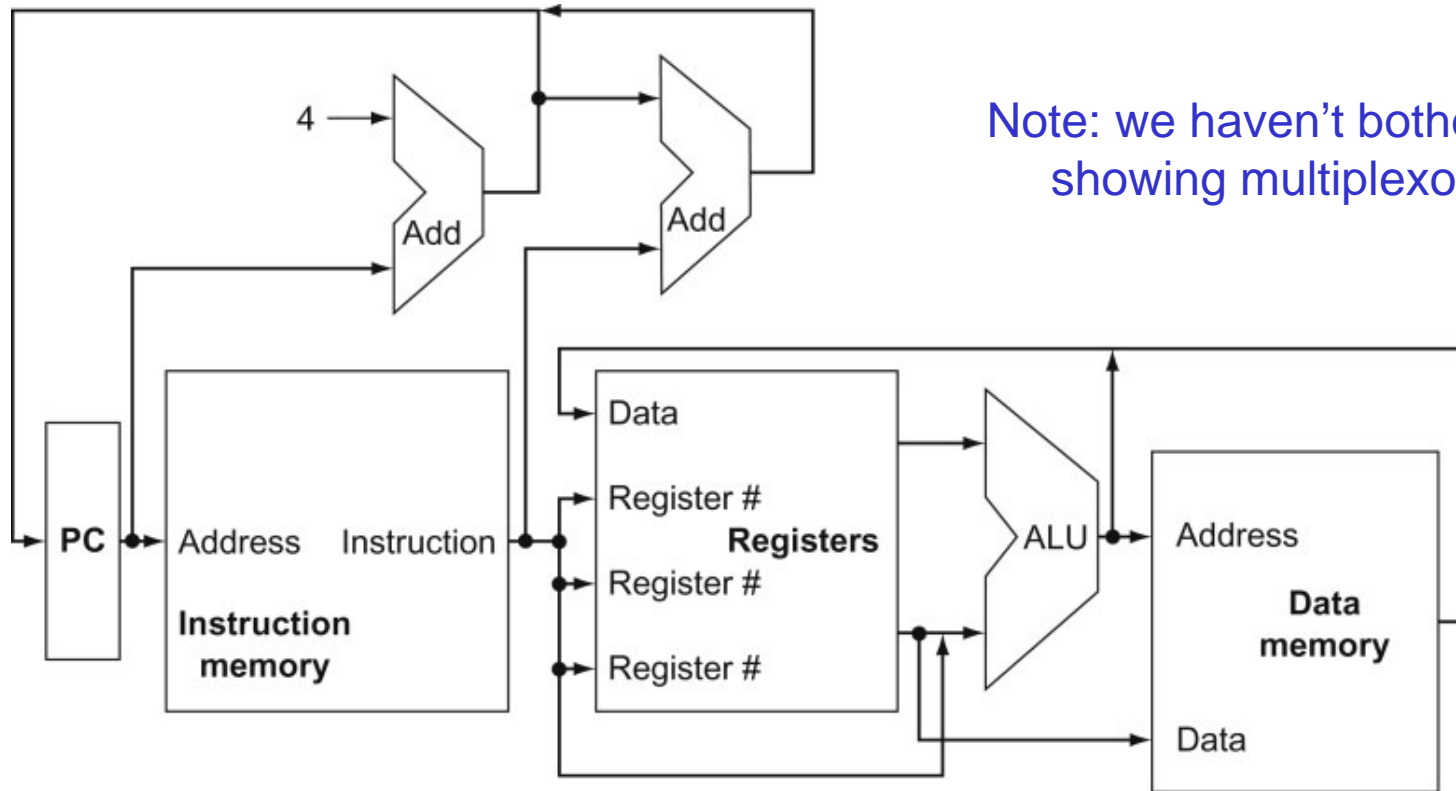


Note: we haven't bothered showing multiplexors

Source: H&P textbook

- What is the role of the Add units?
- Explain the inputs to the data memory unit
- Explain the inputs to the ALU
- Explain the inputs to the register unit

# Clocking Methodology

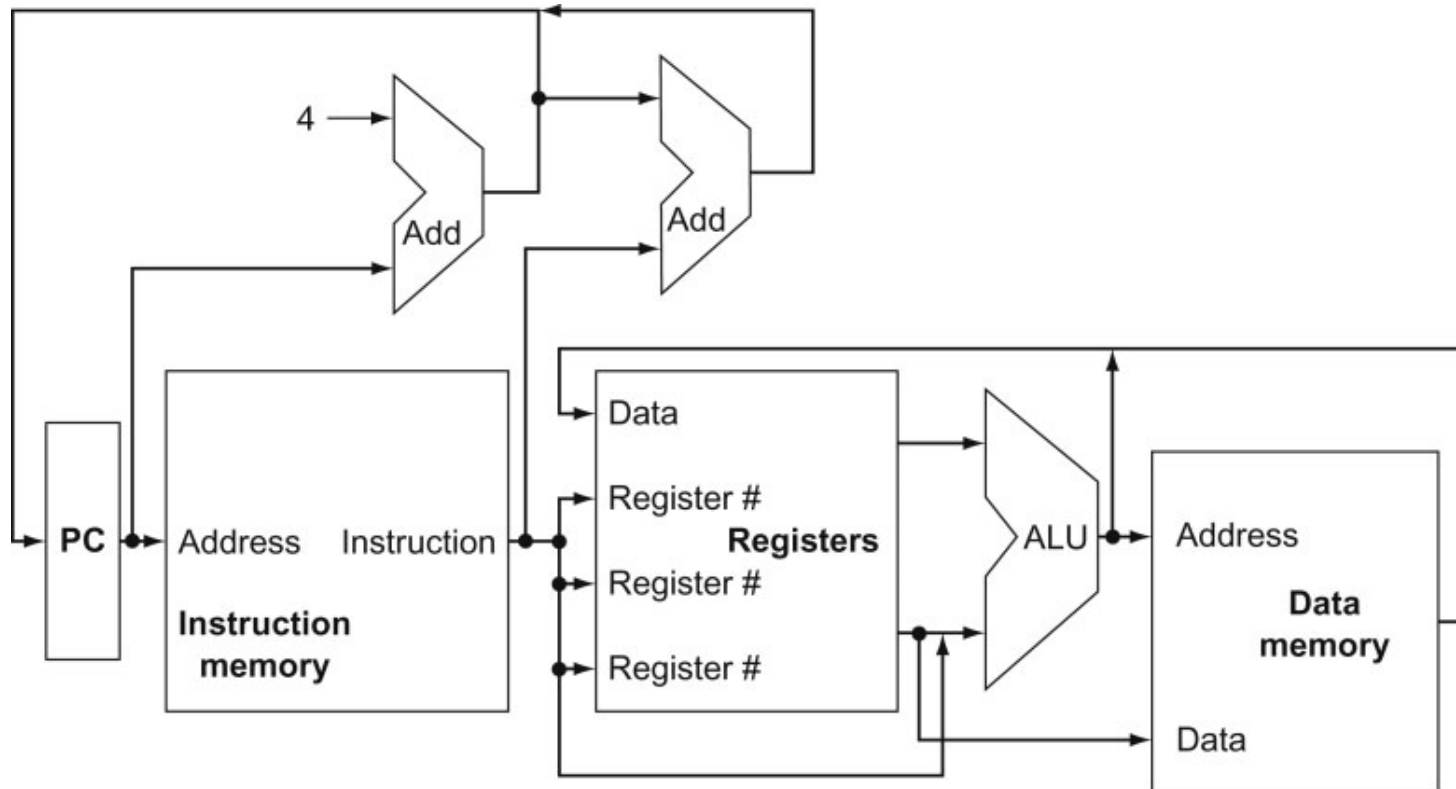

Source: H&P textbook

- Which of the above units need a clock?
  - What is being saved (latched) on the rising edge of the clock?
- Keep in mind that the latched value remains there for an entire cycle

# Title

---

- Bullet