
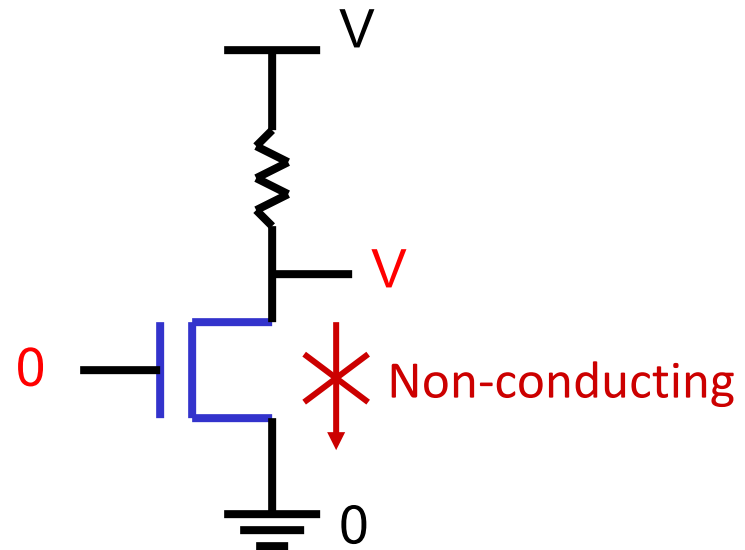


Lecture 12: Hardware for Arithmetic

- Today's topics:
 - Digital logic intro
 - Logic for common operations
 - Designing an ALU

Digital Design Basics

 - Two voltage levels – high and low (1 and 0, true and false)
Hence, the use of binary arithmetic/logic in all computers
- A transistor is a 3-terminal device that acts as a switch



Logic Blocks

- A logic block has a number of binary inputs and produces a number of binary outputs – the simplest logic block is composed of a few transistors
- A logic block is termed *combinational* if the output is only a function of the inputs
- A logic block is termed *sequential* if the block has some internal memory (state) that also influences the output
- A basic logic block is termed a *gate* (AND, OR, NOT, etc.)

We will only deal with combinational circuits today

Truth Table

- A truth table defines the outputs of a logic block for each set of inputs
- Consider a block with 3 inputs A, B, C and an output E that is true only if *exactly* 2 inputs are true

A	B	C	E

Truth Table

- A truth table defines the outputs of a logic block for each set of inputs
- Consider a block with 3 inputs A, B, C and an output E that is true only if *exactly* 2 inputs are true

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Can be compressed by only representing cases that have an output of 1

Boolean Algebra

- Equations involving two values and three primary operators:
 - OR : symbol $+$, $X = A + B \rightarrow$ X is true if at least one of A or B is true
 - AND : symbol \cdot , $X = A \cdot B \rightarrow$ X is true if both A and B are true
 - NOT : symbol $\bar{\quad}$, $X = \bar{A} \rightarrow$ X is the inverted value of A

Boolean Algebra Rules

- Identity law : $A + 0 = A$; $A \cdot 1 = A$
- Zero and One laws : $A + 1 = 1$; $A \cdot 0 = 0$
- Inverse laws : $A \cdot \overline{A} = 0$; $A + \overline{A} = 1$
- Commutative laws : $A + B = B + A$; $A \cdot B = B \cdot A$
- Associative laws : $A + (B + C) = (A + B) + C$
 $A \cdot (B \cdot C) = (A \cdot B) \cdot C$
- Distributive laws : $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$
 $A + (B \cdot C) = (A + B) \cdot (A + C)$

DeMorgan's Laws

- $\overline{A + B} = \overline{A} \cdot \overline{B}$

- $\overline{A \cdot B} = \overline{A} + \overline{B}$

- Confirm that these are indeed true

Pictorial Representations


AND



OR



NOT

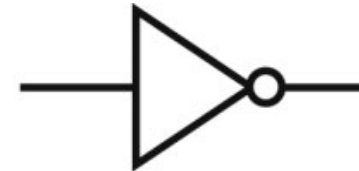

Source: H&P textbook

What logic function is this?



Source: H&P textbook

Boolean Equation

- Consider the logic block that has an output E that is true only if exactly two of the three inputs A, B, C are true

Multiple correct equations:

Two must be true, but all three cannot be true:

$$E = ((A \cdot B) + (B \cdot C) + (A \cdot C)) \cdot \overline{(A \cdot B \cdot C)}$$

Identify the three cases where it is true:

$$E = (A \cdot B \cdot \overline{C}) + (A \cdot C \cdot \overline{B}) + (C \cdot B \cdot \overline{A})$$

Sum of Products

- Can represent any logic block with the AND, OR, NOT operators
 - Draw the truth table
 - For each true output, represent the corresponding inputs as a product
 - The final equation is a sum of these products

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$(A \cdot B \cdot \overline{C}) + (A \cdot C \cdot \overline{B}) + (C \cdot B \cdot \overline{A})$$

- Can also use “product of sums”
- Any equation can be implemented with an array of ANDs, followed by an array of ORs


NAND and NOR

- NAND : NOT of AND : $A \text{ nand } B = \overline{A \cdot B}$
- NOR : NOT of OR : $A \text{ nor } B = \overline{A + B}$
- NAND and NOR are *universal gates*, i.e., they can be used to construct any complex logical function

Common Logic Blocks – Decoder


Takes in N inputs and activates one of 2^N outputs

I_0	I_1	I_2	O_0	O_1	O_2	O_3	O_4	O_5	O_6	O_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

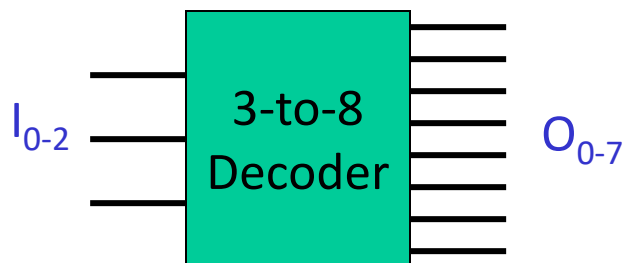

Common Logic Blocks – Multiplexor

 - Multiplexor or selector: one of N inputs is reflected on the output depending on the value of the $\log_2 N$ selector bits




2-input mux

Source: H&P textbook

Adder Algorithm

	1	0	0	1
	0	1	0	1
<hr/>				
Sum	1	1	1	0
Carry	0	0	0	1

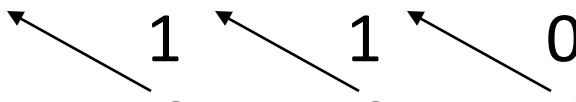

Truth Table for the above operations:

A	B	Cin	Sum	Cout
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Adder Algorithm

	1	0	0	1
	0	1	0	1
Sum	1	1	1	0
Carry	0	0	0	1

Truth Table for the above operations:


A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Equations:

$$\begin{aligned} \text{Sum} &= \text{Cin} \cdot \overline{A} \cdot \overline{B} + \\ &\quad B \cdot \overline{\text{Cin}} \cdot \overline{A} + \\ &\quad A \cdot \overline{\text{Cin}} \cdot \overline{B} + \\ &\quad A \cdot B \cdot \text{Cin} \end{aligned}$$

$$\begin{aligned} \text{Cout} &= A \cdot B \cdot \text{Cin} + \\ &\quad A \cdot B \cdot \overline{\text{Cin}} + \\ &\quad A \cdot \text{Cin} \cdot \overline{B} + \\ &\quad B \cdot \text{Cin} \cdot \overline{A} \\ &= A \cdot B + \\ &\quad A \cdot \text{Cin} + \\ &\quad B \cdot \text{Cin} \end{aligned}$$

Carry Out Logic

 

Equations:


$$\begin{aligned} \text{Sum} &= \text{Cin} \cdot \bar{A} \cdot \bar{B} + \\ &\quad B \cdot \bar{\text{Cin}} \cdot \bar{A} + \\ &\quad A \cdot \bar{\text{Cin}} \cdot B + \\ &\quad A \cdot B \cdot \text{Cin} \end{aligned}$$

$$\begin{aligned} \text{Cout} &= A \cdot B \cdot \text{Cin} + \\ &\quad A \cdot B \cdot \bar{\text{Cin}} + \\ &\quad A \cdot \text{Cin} \cdot \bar{B} + \\ &\quad B \cdot \text{Cin} \cdot \bar{A} \\ &= A \cdot B + \\ &\quad A \cdot \text{Cin} + \\ &\quad B \cdot \text{Cin} \end{aligned}$$

Source: H&P textbook

1-Bit ALU with Add, Or, And

 
- Multiplexor selects between Add, Or, And operations



Source: H&P textbook

32-bit Ripple Carry Adder

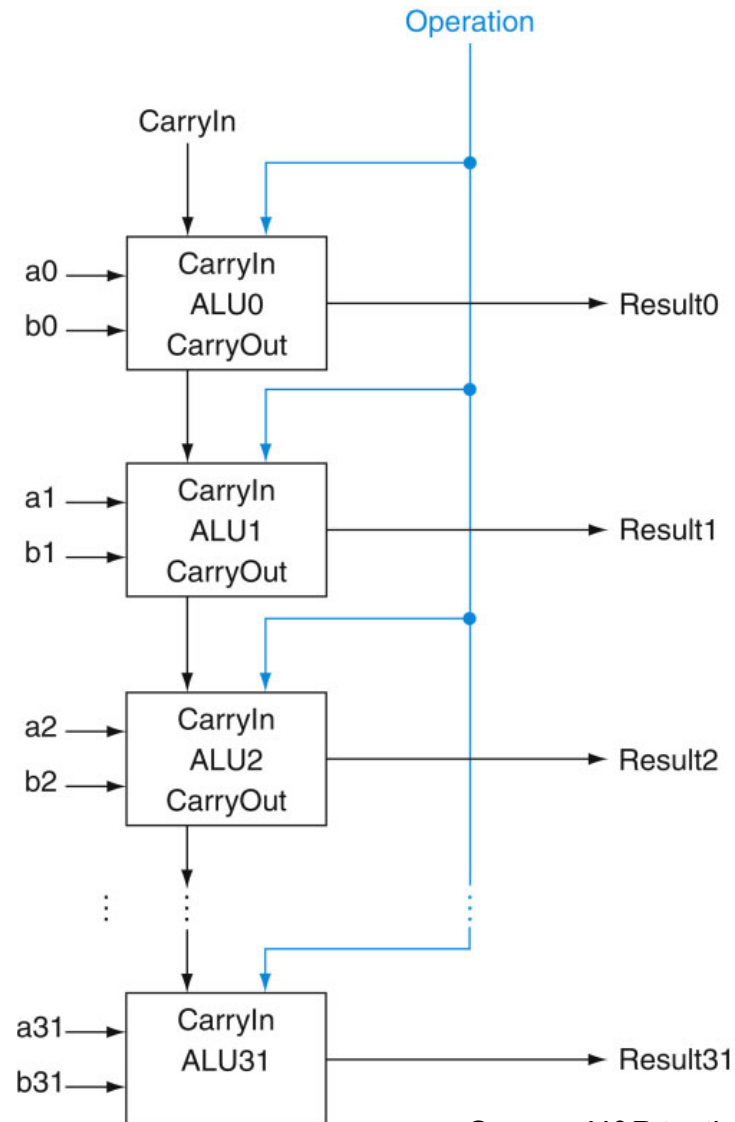1-bit ALUs are connected “in series” with the carry-out of 1 box going into the carry-in of the next box




Source: H&P textbook

Incorporating Subtraction


Must invert bits of B and add a 1

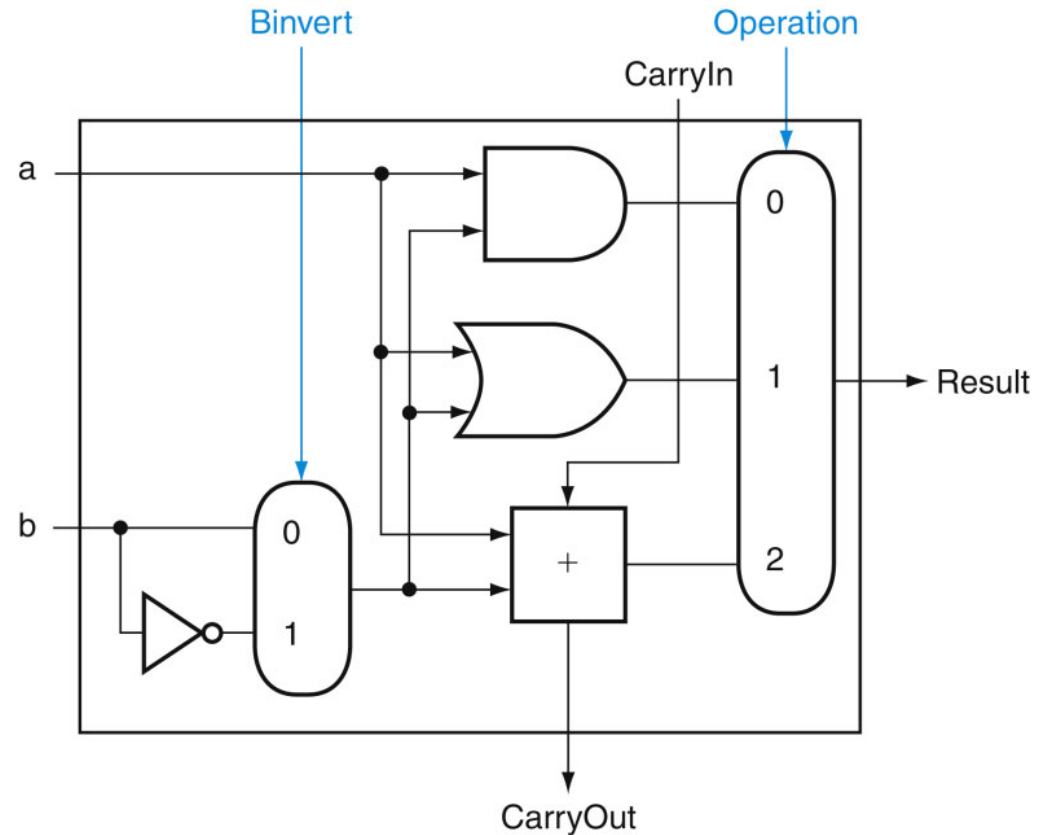- Include an inverter
- CarryIn for the first bit is 1
- The CarryIn signal (for the first bit) can be the same as the Binvert signal



Source: H&P textbook

Incorporating NOR and NAND

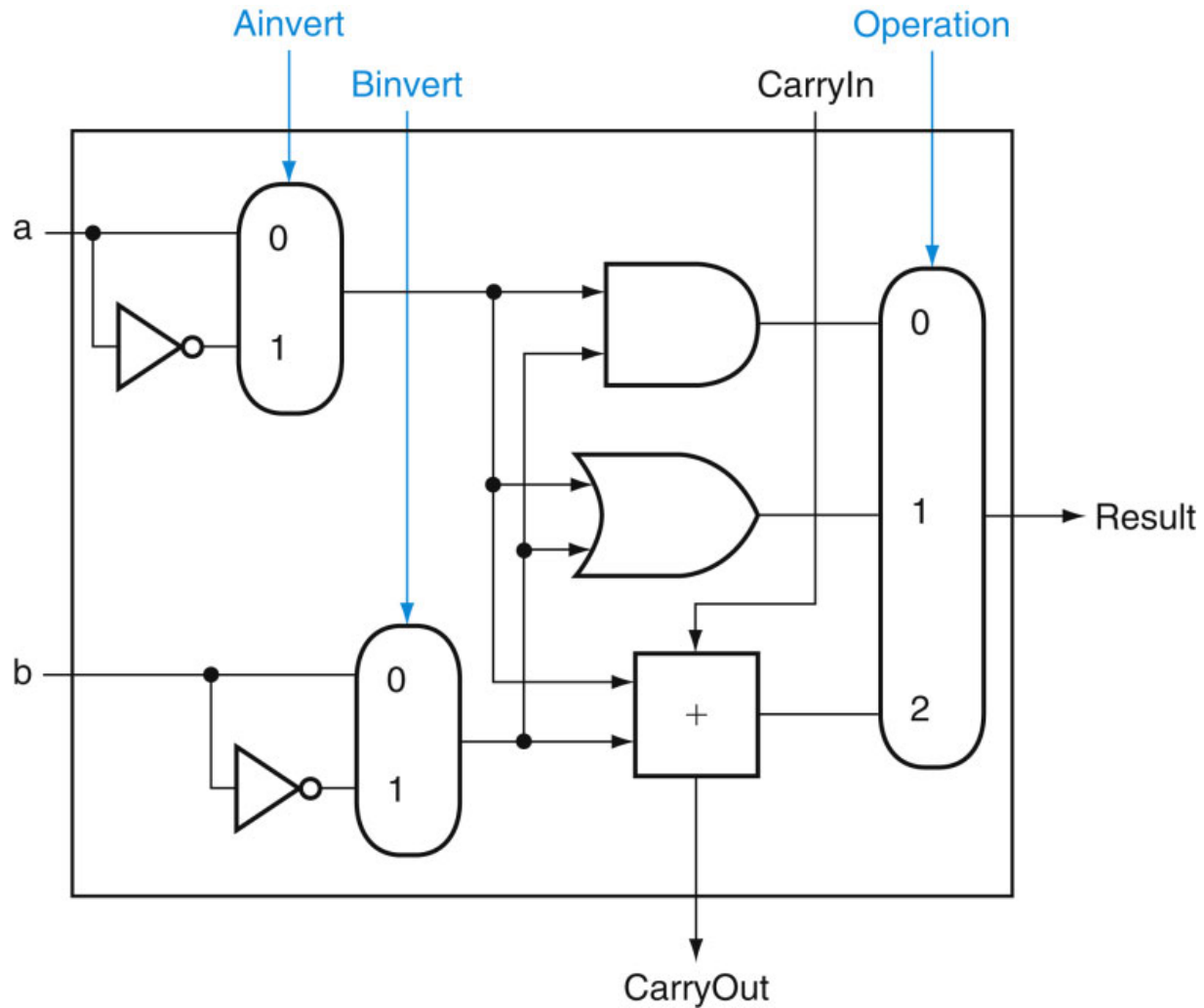

Control Lines

What are the values of the control lines and what operations do they correspond to?

	Ai	Bn	Op
AND	0	0	00
OR	0	0	01
Add	0	0	10
Sub	0	1	10
NAND	1	1	01
NOR	1	1	00

