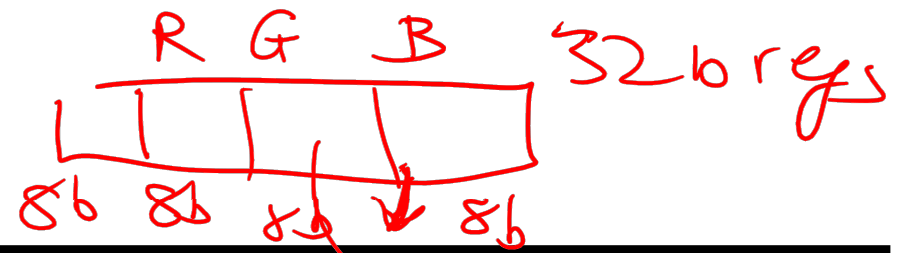


Lecture 12: Hardware for Arithmetic

- Today's topics:
 - Digital logic intro
 - Logic for common operations
 - Designing an ALU

Subword Parallelism





- ALUs are typically designed to perform 64-bit or 128 bit arithmetic
- Some data types are much smaller, e.g., bytes for pixel RGB values, half-words for audio samples
- Partitioning the carry-chains within the ALU can convert the 64-bit adder into 4 16-bit adders or 8 8-bit adders
- A single load can fetch multiple values, and a single add instruction can perform multiple parallel additions, referred to as subword parallelism

ALU
SP
↓
SIMD
Vector

Digital Design Basics

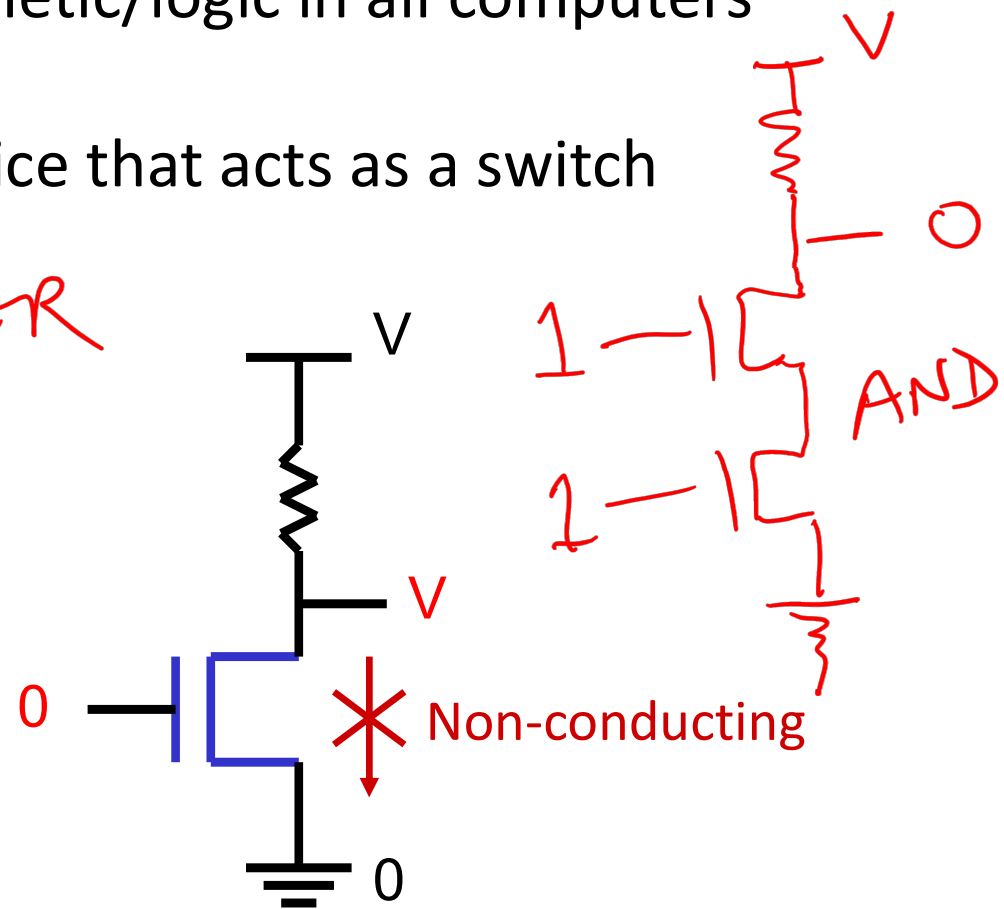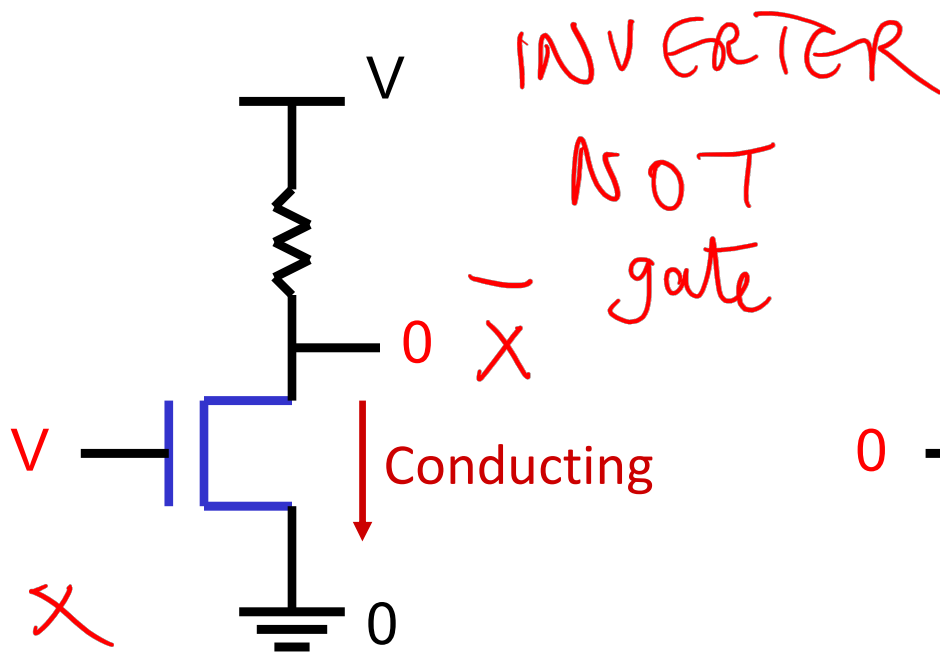- Two voltage levels – high and low (1 and 0, true and false)
Hence, the use of binary arithmetic/logic in all computers
- A transistor is a 3-terminal device that acts as a switch




Logic Blocks

- A logic block has a number of binary inputs and produces a number of binary outputs – the simplest logic block is composed of a few transistors
- A logic block is termed *combinational* if the output is only a function of the inputs
- A logic block is termed *sequential* if the block has some internal memory (state) that also influences the output
- A basic logic block is termed a *gate* (AND, OR, NOT, etc.)

We will only deal with combinational circuits today

Truth Table

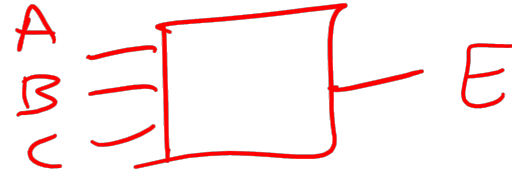


- A truth table defines the outputs of a logic block for each set of inputs
- Consider a block with 3 inputs A, B, C and an output E that is true only if exactly 2 inputs are true

Dec #	A	B	C	E
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Truth Table

- A truth table defines the outputs of a logic block for each set of inputs
- Consider a block with 3 inputs A, B, C and an output E that is true only if *exactly* 2 inputs are true

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

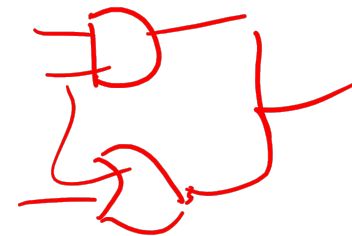

Can be compressed by only representing cases that have an output of 1

Boolean Algebra

- Equations involving two values and three primary operators:
 - OR : symbol + , $X = A + B$ $\rightarrow$ X is true if at least one of A or B is true
 - AND : symbol . , $X = A . B$ $\rightarrow$ X is true if both A and B are true
 - NOT : symbol $\bar{}$, $X = \bar{A}$ $\rightarrow$ X is the inverted value of A

Boolean Algebra Rules

- Identity law : $A + 0 = A$; $A \cdot 1 = A$
- Zero and One laws : $A + 1 = 1$; $A \cdot 0 = 0$
- Inverse laws : $A \cdot \bar{A} = 0$; $A + \bar{A} = 1$
- Commutative laws : $A + B = B + A$; $A \cdot B = B \cdot A$
- Associative laws : $A + (B + C) = (A + B) + C$
 $A \cdot (B \cdot C) = (A \cdot B) \cdot C$
- Distributive laws : $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$
 $A + (B \cdot C) = (A + B) \cdot (A + C)$

DeMorgan's Laws

- $\overline{A + B} = \overline{A} \cdot \overline{B}$ 

- $\overline{A \cdot B} = \overline{A} + \overline{B}$ 


- Confirm that these are indeed true

Pictorial Representations


NAND




AND

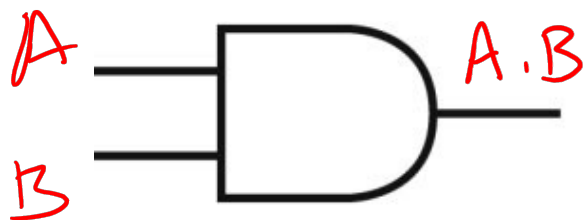

OR

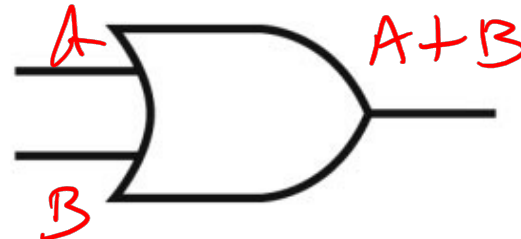


NOT

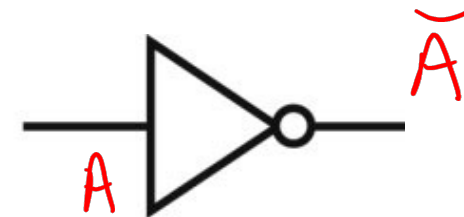

Source: H&P textbook

What logic function is this?

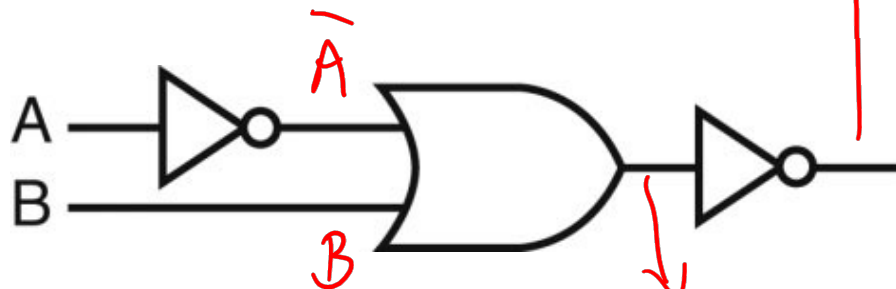

$\bar{A} + B$

$$\begin{aligned}\overline{\bar{A} + B} &= \bar{\bar{A}} \cdot \bar{B} \\ &= A \cdot \bar{B}\end{aligned}$$



Source: H&P textbook

NOR

Boolean Equation

- Consider the logic block that has an output E that is true only if exactly two of the three inputs A, B, C are true

Multiple correct equations:

Two must be true, but all three cannot be true:

$$E = ((A \cdot B) + (B \cdot C) + (A \cdot C)) \cdot \overline{(A \cdot B \cdot C)}$$

Identify the three cases where it is true:

$$E = (A \cdot B \cdot \overline{C}) + (A \cdot C \cdot \overline{B}) + (C \cdot B \cdot \overline{A})$$

Sum of Products

prod of sums:

$$(\bar{A} + \bar{B} + \bar{C}) \cdot (\bar{A} + B + C) \cdot (A + \bar{B} + C) \cdot (A + B + \bar{C})$$

- Can represent any logic block with the AND, OR, NOT operators
 - Draw the truth table
 - For each true output, represent the corresponding inputs as a product
 - The final equation is a sum of these products

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$\bar{A} \cdot B \cdot C$
sum of prod

$(A \cdot B \cdot \bar{C}) + (A \cdot C \cdot \bar{B}) + (C \cdot B \cdot \bar{A})$

- Can also use “product of sums”
- Any equation can be implemented with an array of ANDs, followed by an array of ORs

NAND and NOR






- NAND : NOT of AND : $A \text{ nand } B = \overline{A \cdot B}$
- NOR : NOT of OR : $A \text{ nor } B = \overline{A + B}$
- NAND and NOR are universal gates, i.e., they can be used to construct any complex logical function

Common Logic Blocks – Decoder

$$O_0 \Rightarrow \overline{I_0} \cdot \overline{I_1} \cdot \overline{I_2}$$

Takes in N inputs and activates one of 2^N outputs


I_0	I_1	I_2	O_0	O_1	O_2	O_3	O_4	O_5	O_6	O_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

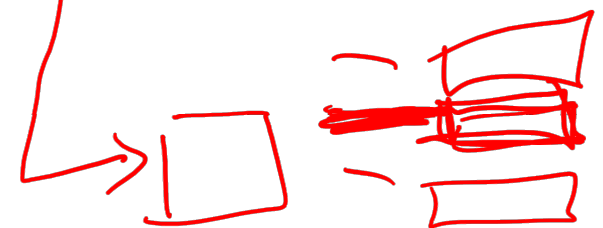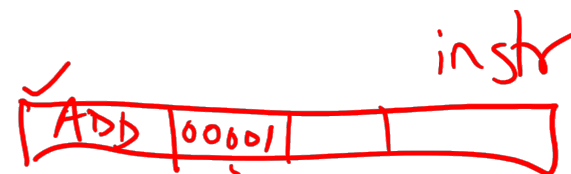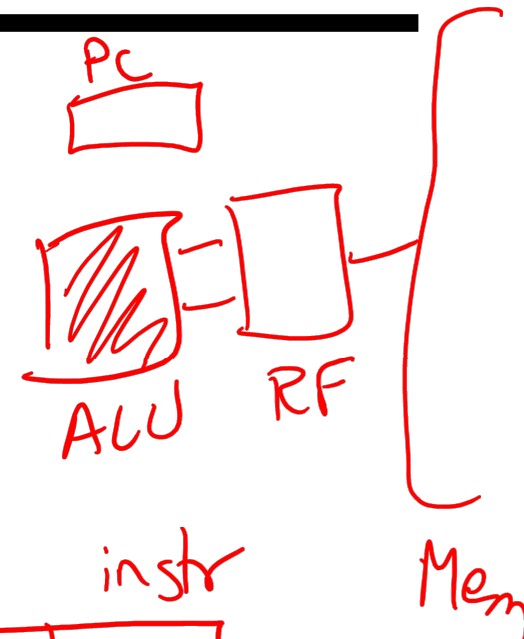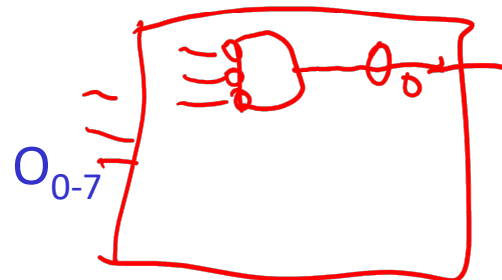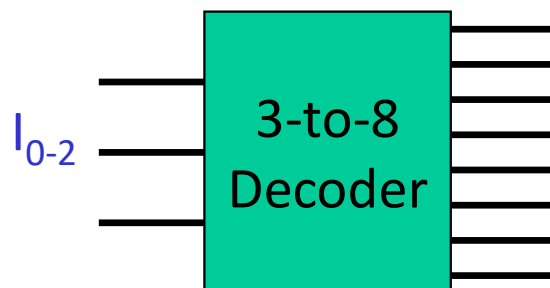



5-to-32
dec




Common Logic Blocks – Multiplexor

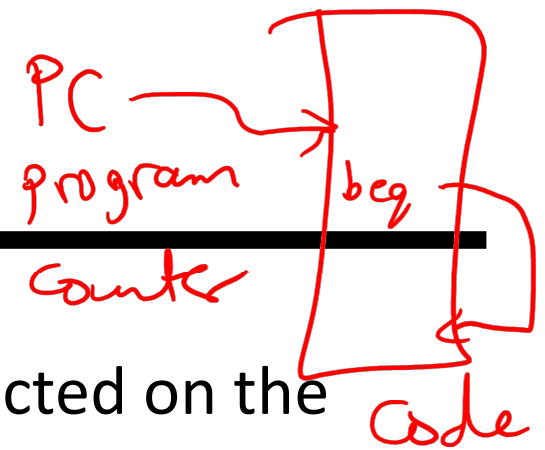

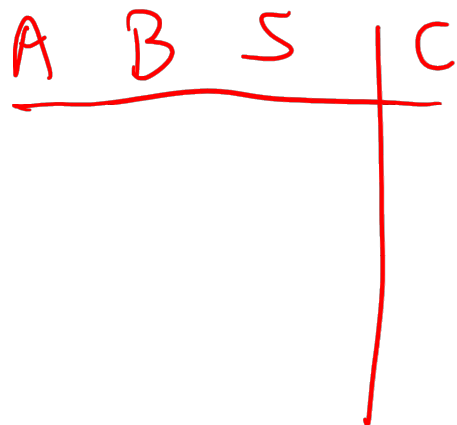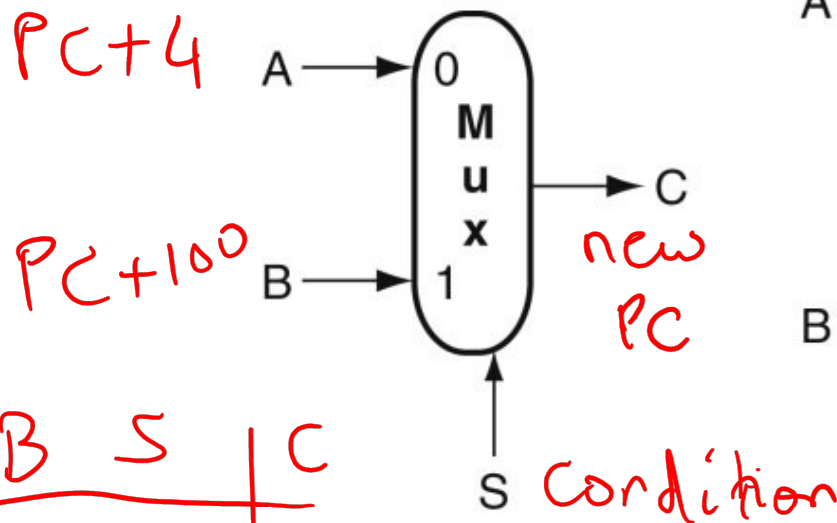- Multiplexor or selector: one of N inputs is reflected on the output depending on the value of the $\log_2 N$ selector bits



2-input mux
[S]B

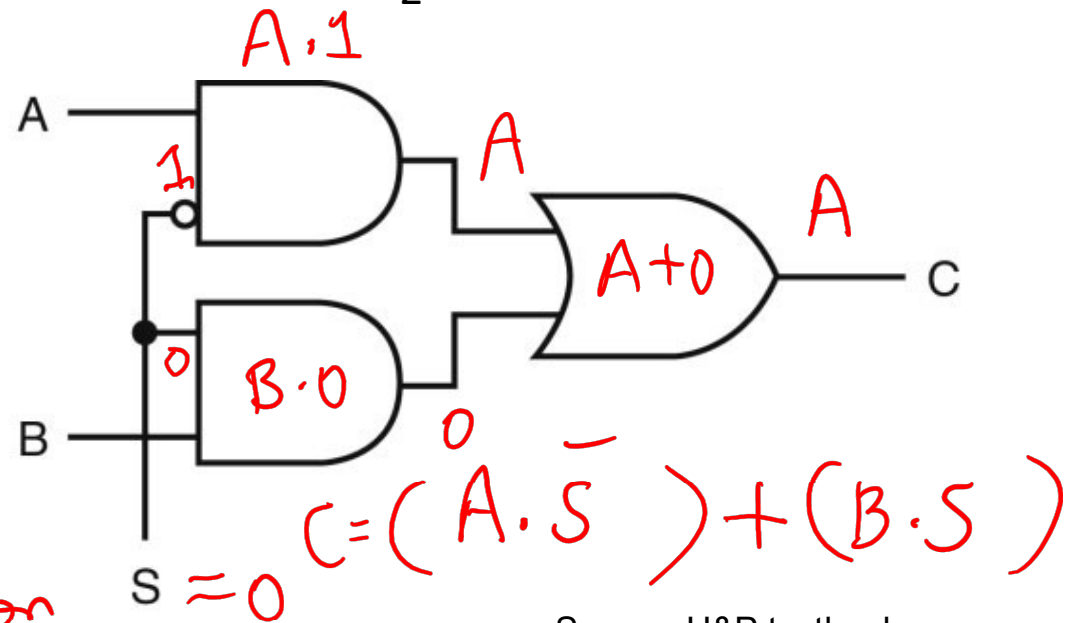


Source: H&P textbook

$$C = A \text{ if } S = 0$$

$$C = B \text{ if } S = 1$$


Adder Algorithm

	0	0	1	1
	1	0	0	1
	0	1	0	1
Sum	1	1	1	0
Carry	0	0	0	1

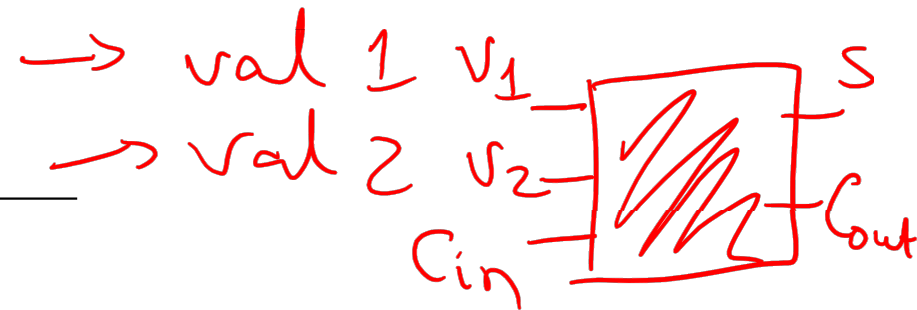

Truth Table for the above operations:

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

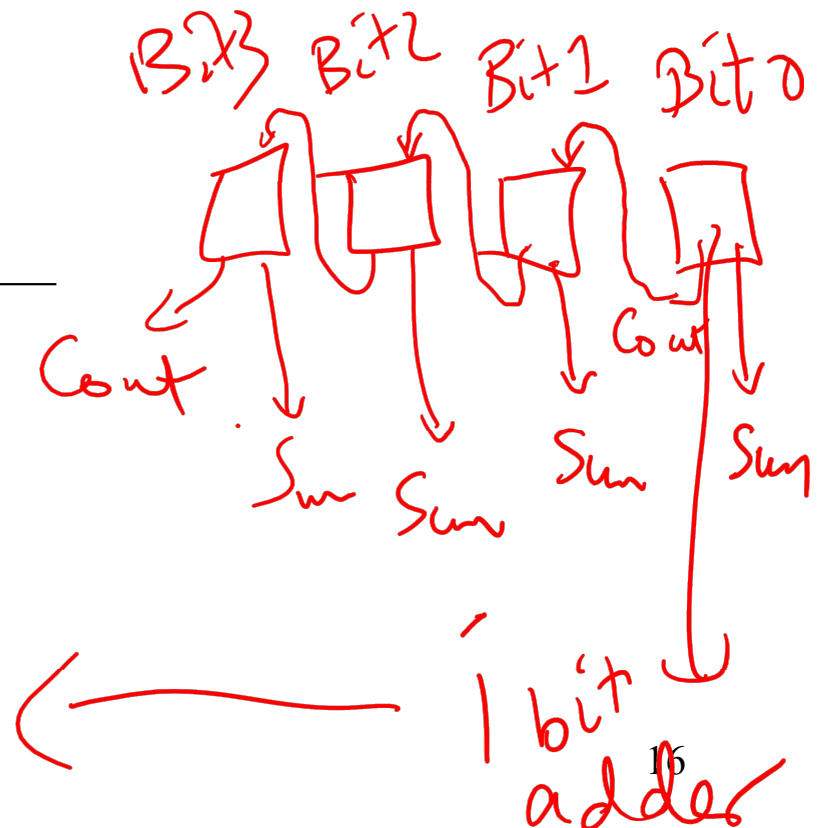

Adder Algorithm

	1	0	0	1
	0	1	0	1
Sum	1	1	1	0
Carry	0	0	0	1

Equations:


$$\begin{aligned} \text{Sum} = & \text{Cin} \cdot \bar{A} \cdot \bar{B} + \\ & B \cdot \bar{\text{Cin}} \cdot \bar{A} + \\ & A \cdot \bar{\text{Cin}} \cdot B + \\ & A \cdot B \cdot \text{Cin} \end{aligned}$$

Truth Table for the above operations:

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned} \text{Cout} = & A \cdot B \cdot \text{Cin} + \\ & A \cdot B \cdot \bar{\text{Cin}} + \\ & A \cdot \text{Cin} \cdot \bar{B} + \\ & B \cdot \text{Cin} \cdot \bar{A} \\ = & A \cdot B + \\ & A \cdot \text{Cin} + \\ & B \cdot \text{Cin} \end{aligned}$$

Carry Out Logic

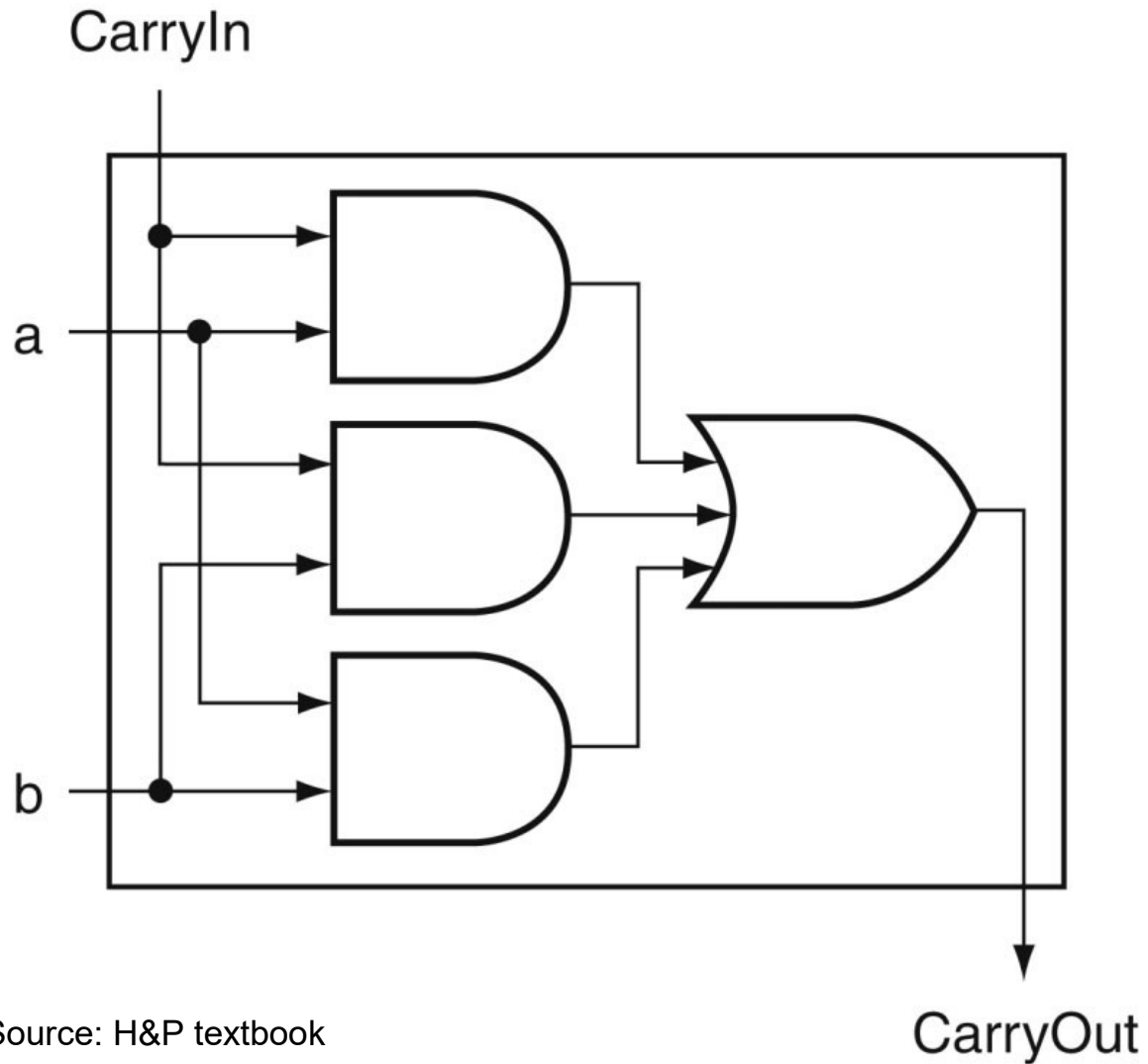

Equations:


$$\begin{aligned} \text{Sum} = & \text{Cin} \cdot \bar{A} \cdot \bar{B} + \\ & B \cdot \bar{\text{Cin}} \cdot \bar{A} + \\ & A \cdot \bar{\text{Cin}} \cdot B + \\ & A \cdot B \cdot \text{Cin} \end{aligned}$$

$$\begin{aligned} \text{Cout} = & A \cdot B \cdot \text{Cin} + \\ & A \cdot B \cdot \bar{\text{Cin}} + \\ & A \cdot \text{Cin} \cdot \bar{B} + \\ & B \cdot \text{Cin} \cdot \bar{A} \\ = & A \cdot B + \\ & A \cdot \text{Cin} + \\ & B \cdot \text{Cin} \end{aligned}$$

Source: H&P textbook

1-Bit ALU with Add, Or, And

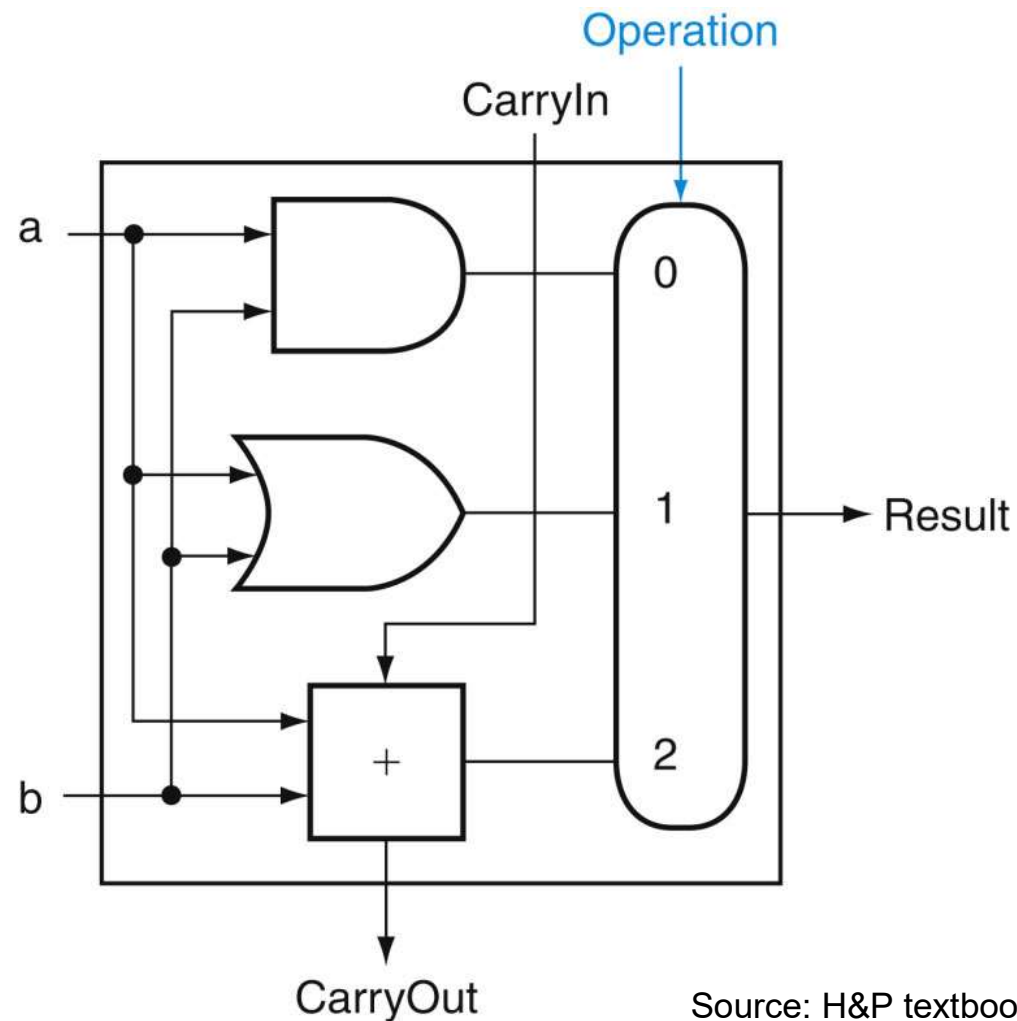
- Multiplexor selects between Add, Or, And operations



Source: H&P textbook

32-bit Ripple Carry Adder

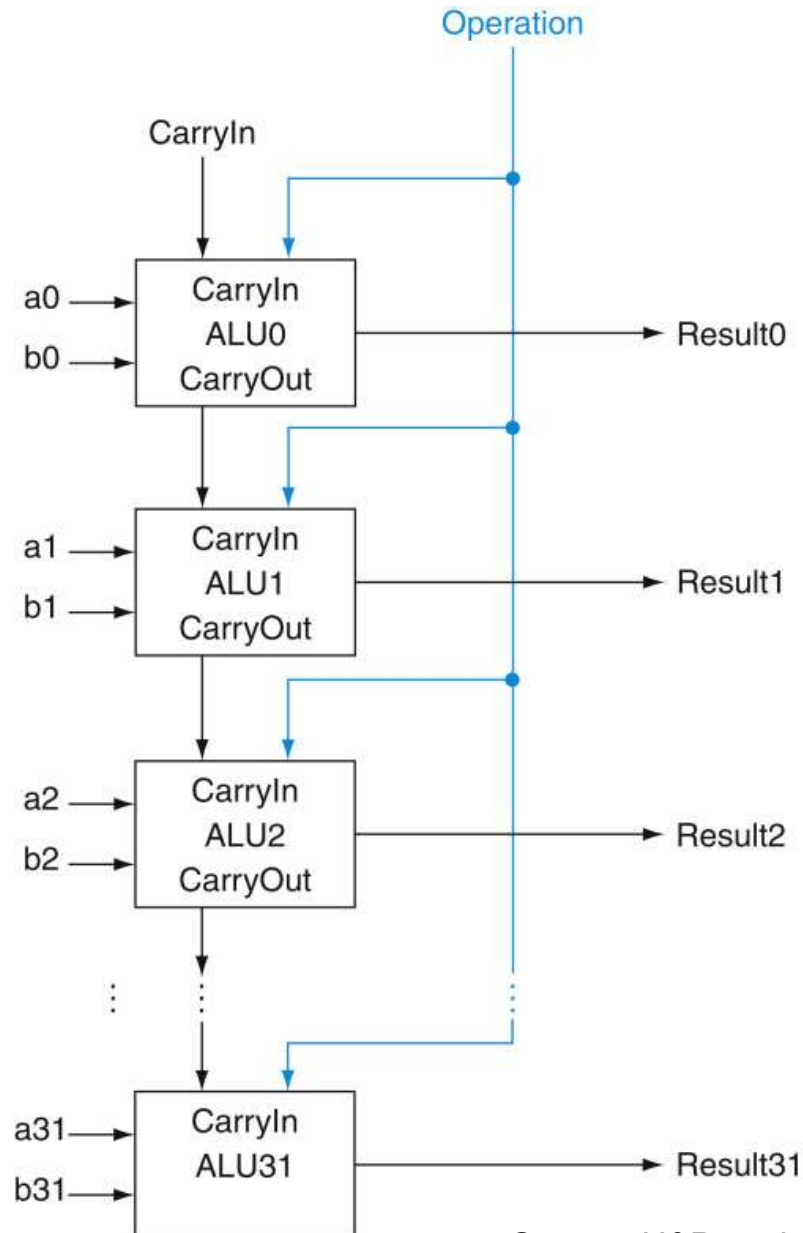1-bit ALUs are connected
“in series” with the
carry-out of 1 box
going into the carry-in
of the next box



Source: H&P textbook