

Lecture 15: Basic CPU Design



- Today's topics:
 - FSM examples
 - Single-cycle CPU
 - ~~Multi-cycle CPU~~

State Diagram

states: N, E
input: EWwait, NSwait

State Transition Table:

CurrState	InputEW	InputNS	NextState=Output
N	0	0	N
N	0	1	N
N	1	0	E
N	1	1	E
E	0	0	E
E	0	1	N
E	1	0	E
E	1	1	N

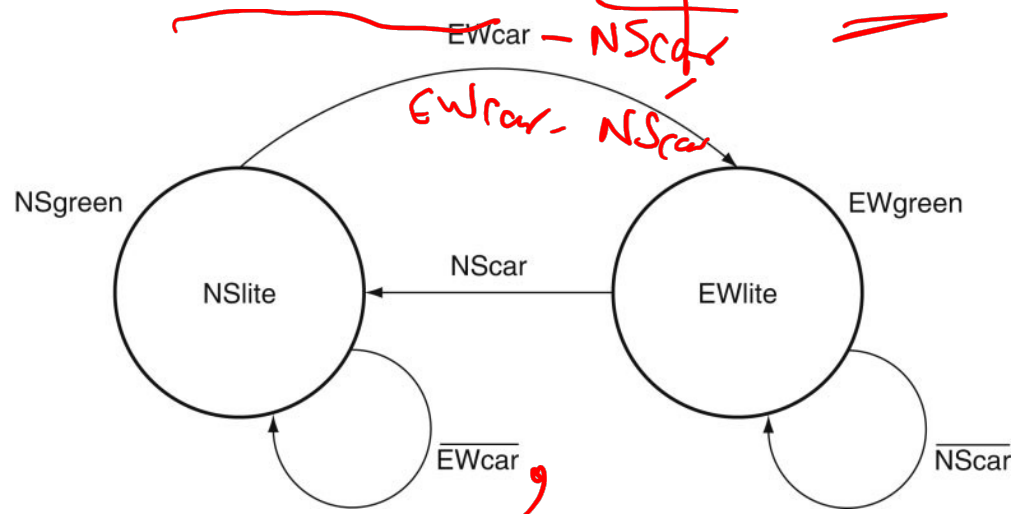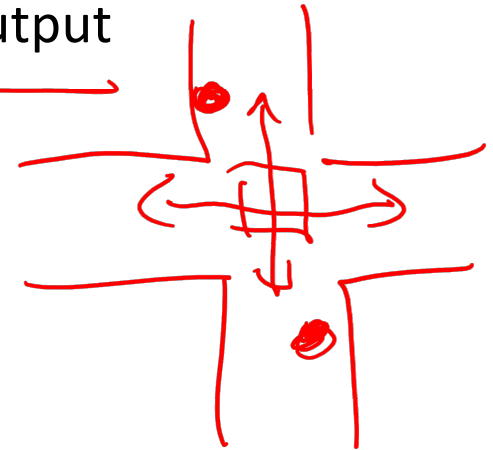

Tackling FSM Problems

- Three questions worth asking:

- ■ What are the possible output states? Draw a bubble for each.
- ■ What are inputs? What values can those inputs take?
- ■ For each state, what do I do for each possible input value? Draw an arc out of every bubble for every input value.

3 values H, C, E

2 vals D, U

3

Curstate	IT	ET

Example – Residential Thermostat

- Two temp sensors: internal and external
- If internal temp is within 1 degree of desired, don't change setting
- • If internal temp is > 1 degree higher than desired, turn AC on; if internal temp is < 1 degree lower than desired, turn heater on
- If external temp and desired temp are within 5 degrees, disregard the internal temp, and turn both AC and heater off


2 inputs What are inputs?
Int Th Ext Th
H G C D U
what values from input sensors?

What are the output states?
AC-on, Heater-on, All-off

Finite State Machine Table

Current State	Input E	Input I	Output State
HEAT	D	C	OFF
HEAT	D	G	OFF
HEAT	D	H	OFF
HEAT	U	C	HEAT
HEAT	U	G	HEAT
HEAT	U	H	COOL
COOL	D	C	OFF
COOL	D	G	OFF
COOL	D	H	OFF
COOL	U	C	HEAT
COOL	U	G	COOL
COOL	U	H	COOL
OFF	D	C	OFF
OFF	D	G	OFF
OFF	D	H	OFF
OFF	U	C	HEAT
OFF	U	G	OFF
OFF	U	H	COOL

Finite State Diagram

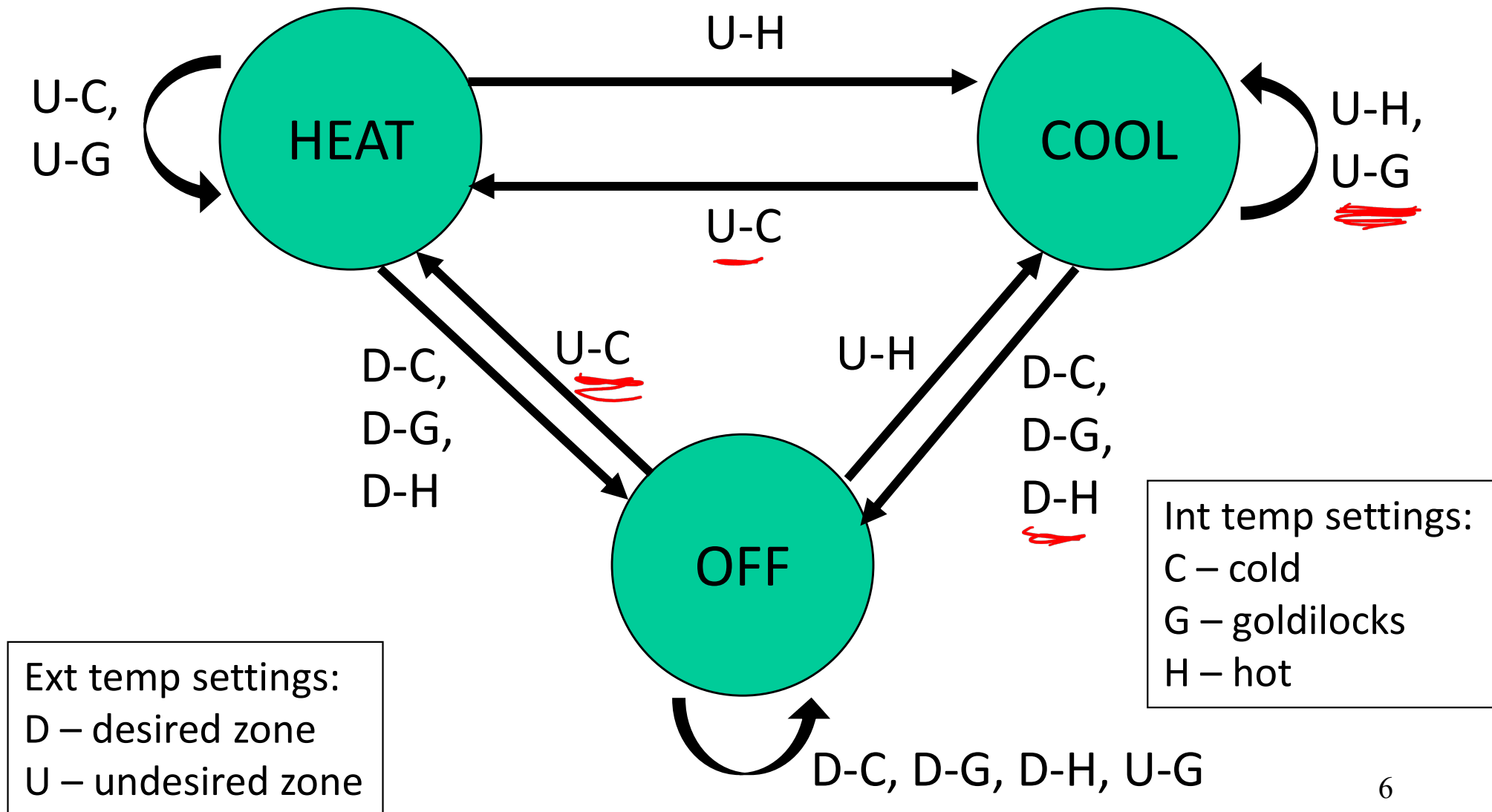

Lazy crocodile Latch vs. Flip-Flop → *Snapping crocodile*

- Recall that we want a circuit to have stable inputs for an entire cycle – so I want my new inputs to arrive at the start of a cycle and be fixed for an entire cycle
- A flip-flop provides the above semantics (a door that swings open and shut at the start of a cycle)
- But a flip-flop needs two back-to-back D-latches, i.e., more transistors, delay, power
- You can reduce these overheads with just a single D-latch (a door that is open for half a cycle) as long as you can tolerate stable inputs for just half a cycle

Basic MIPS Architecture

- Now that we understand clocks and storage of states, we'll design a simple CPU that executes:
 - basic math (add, sub, and, or, slt)
 - memory access (lw and sw)
 - branch and jump instructions (beq and j)


Implementation Overview




- We need memory / cache (fast)
 - to store instructions
 - to store data
 - for now, let's make them separate units



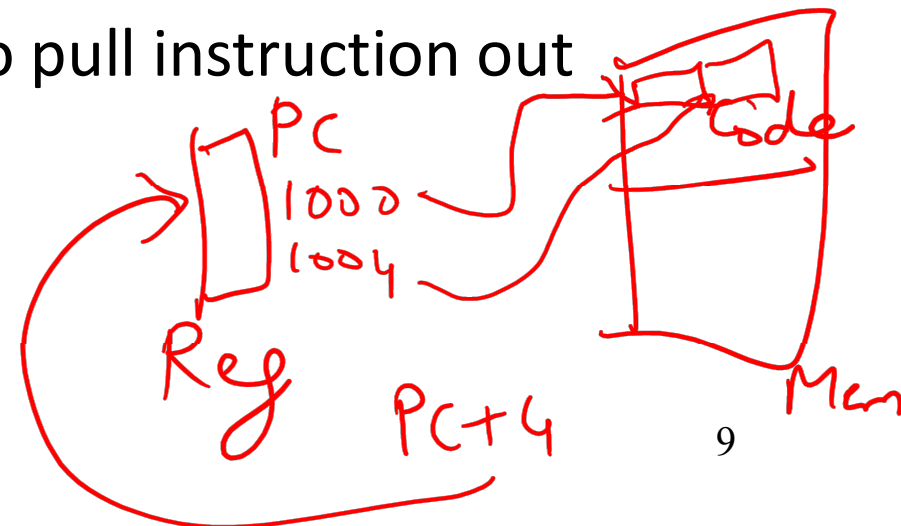- We need registers, ALU, and a whole lot of control logic
- CPU operations common to all instructions:
 - use the program counter (PC) to pull instruction out of instruction memory
 - read register values




View from 30,000 Feet

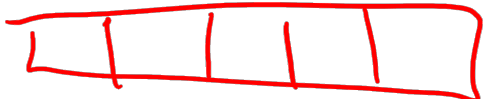
addi \$t3, \$s1, 500

beq \$s1, \$s2, Label

op | s1 | s2 | offset

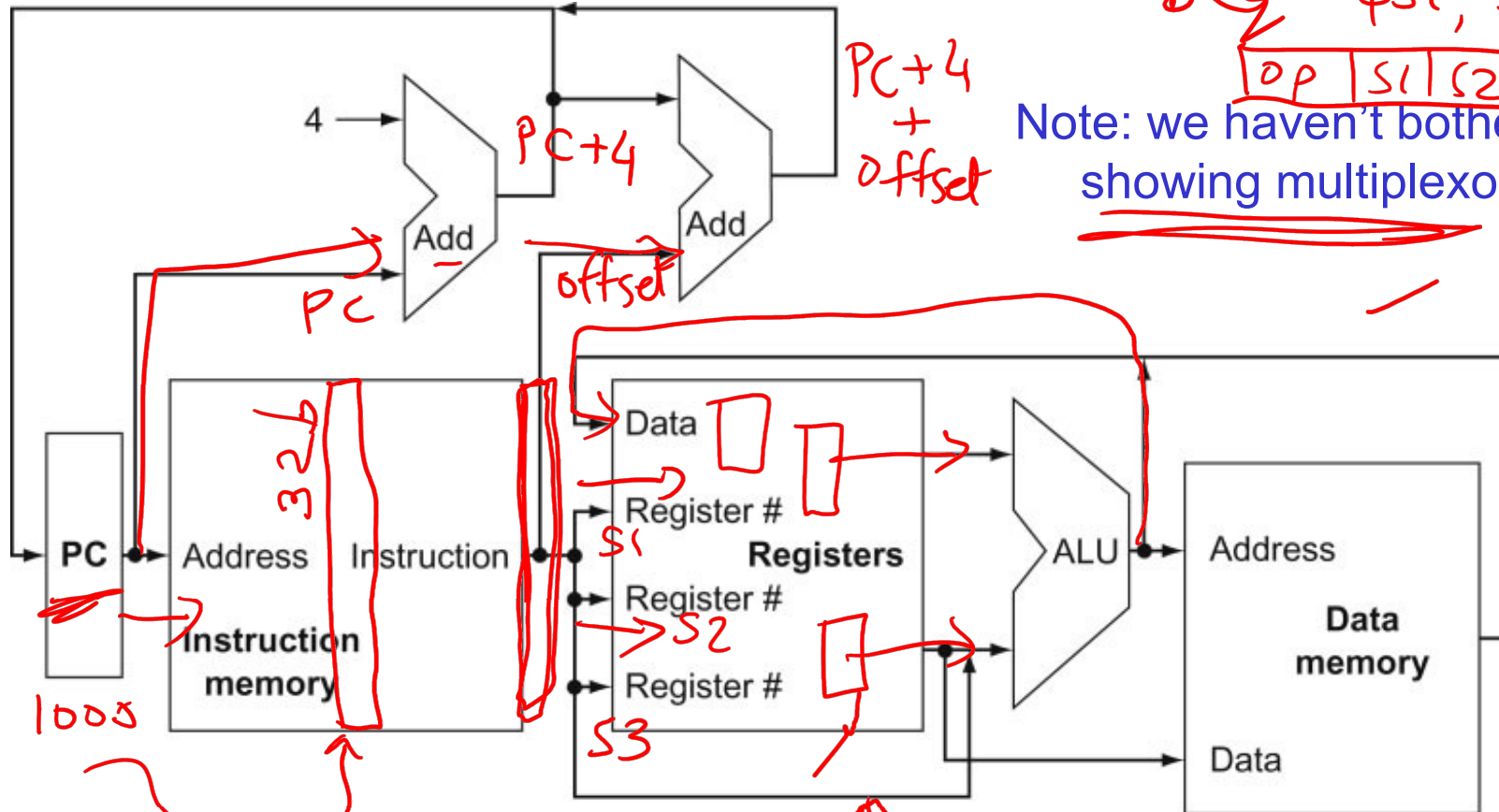Note: we haven't bothered
showing multiplexors




Source: H&P textbook

What is the role of the Add units?

- Explain the inputs to the data memory unit
- Explain the inputs to the ALU *reg, immedi*
- Explain the inputs to the register unit

View from 30,000 Feet

lw \$s1, 8(\$gp)

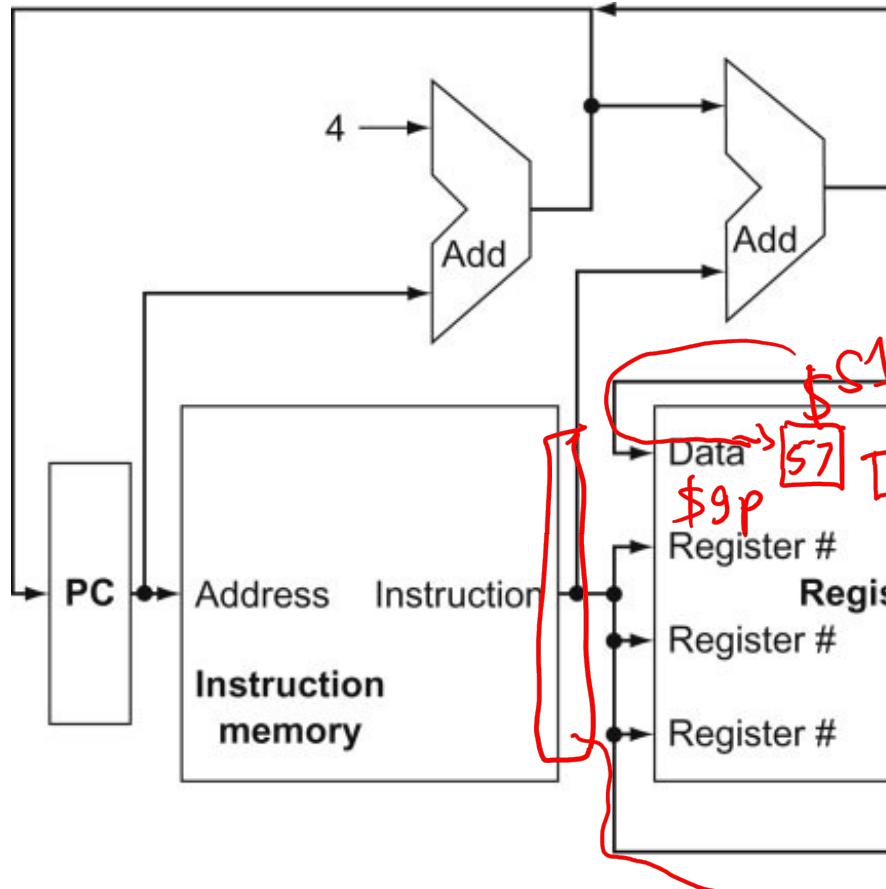


sw \$s1, 8(\$gp)

Note: we haven't bothered showing multiplexors

- What is the role of the Add units?
- Explain the inputs to the data memory unit
- Explain the inputs to the ALU
- Explain the inputs to the register unit

Source: H&P textbook

Clocking Methodology

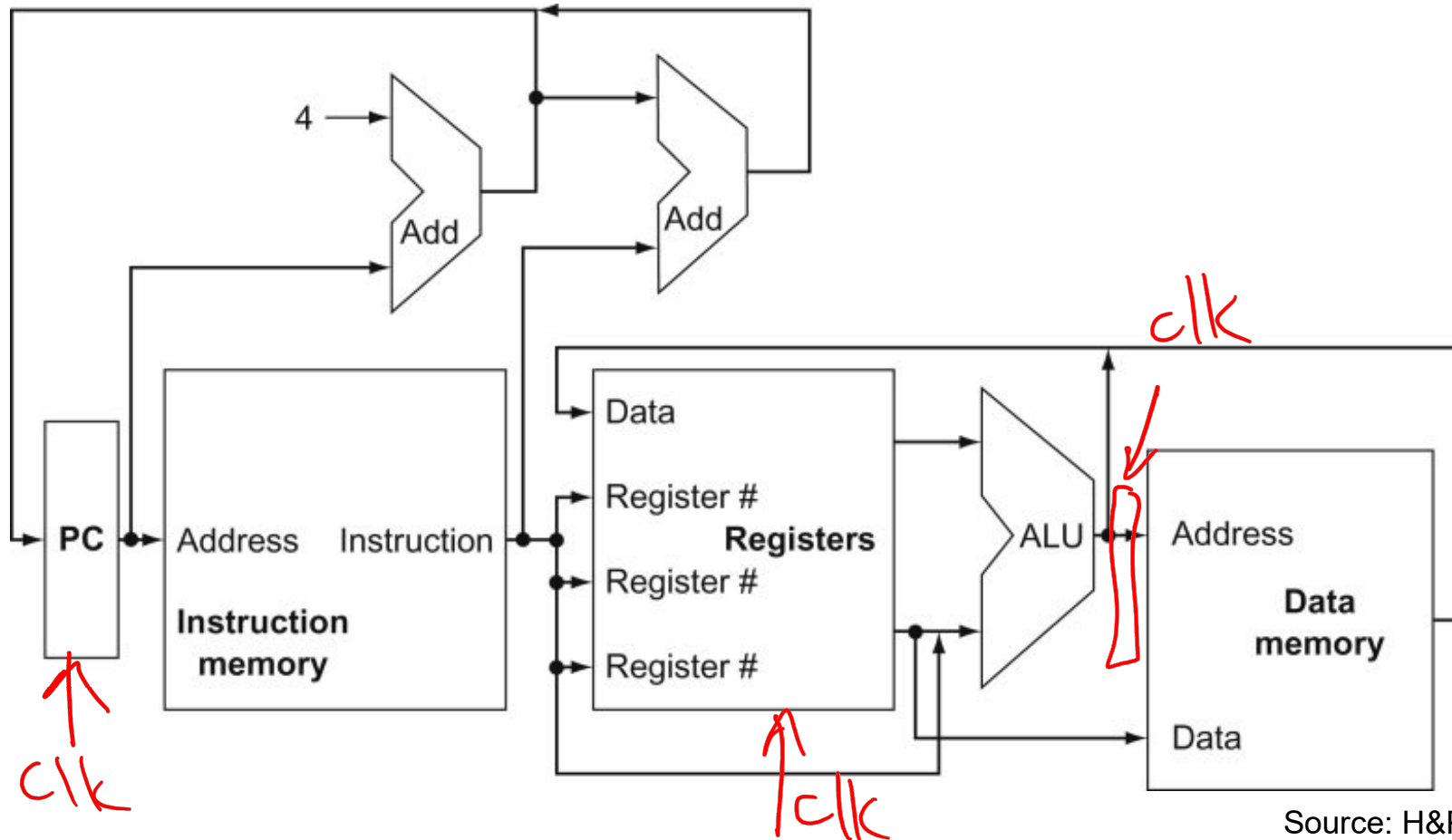


Source: H&P textbook

- Which of the above units need a clock?
- What is being saved (latched) on the rising edge of the clock?
Keep in mind that the latched value remains there for an entire cycle

Implementing R-type Instructions

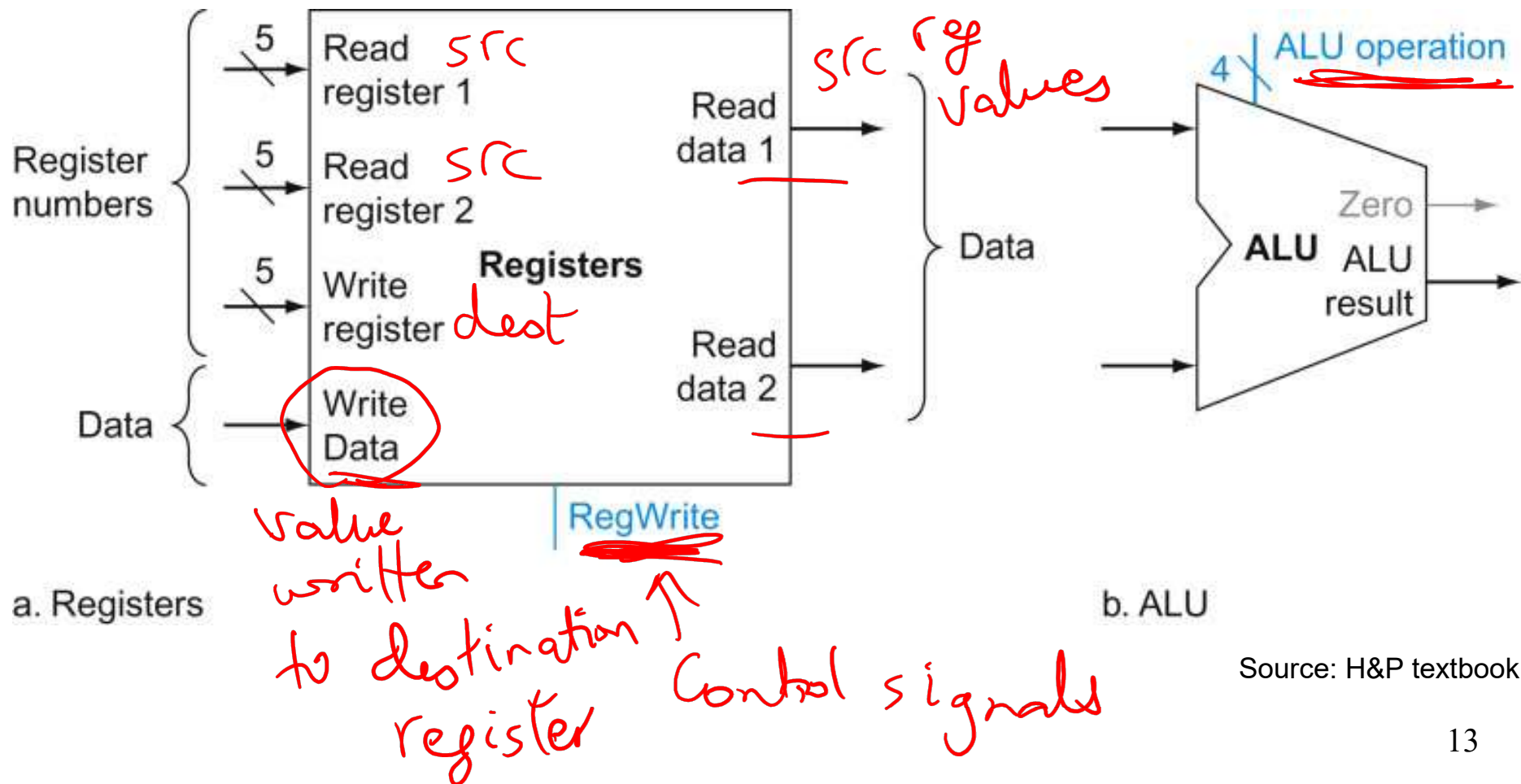
- Instructions of the form add \$t1, \$t2, \$t3
- Explain the role of each signal



Source: H&P textbook


Implementing Loads/Stores

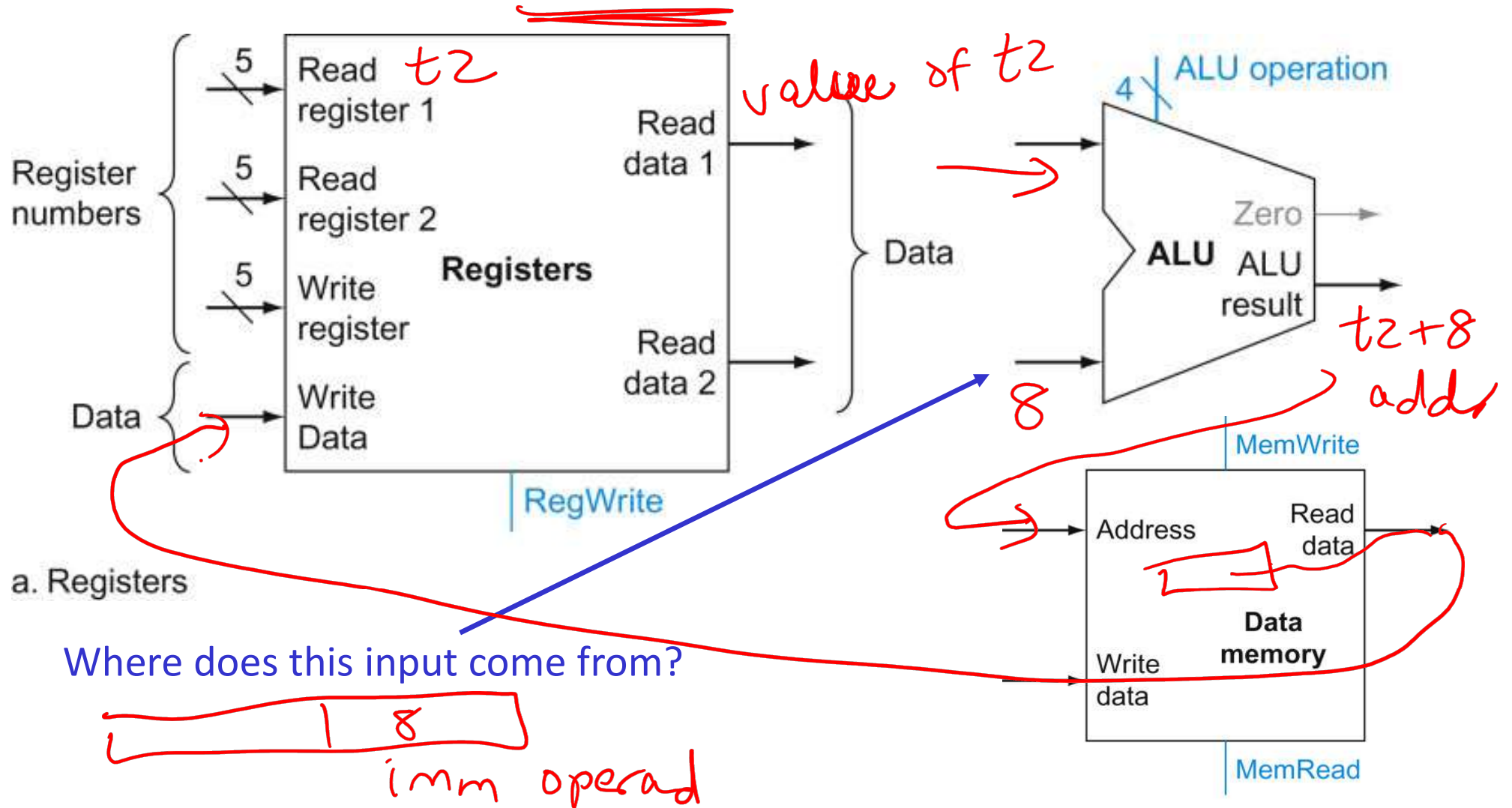- Instructions of the form lw \$t1, 8(\$t2) and sw \$t1, 8(\$t2)




Implementing Loads/Stores

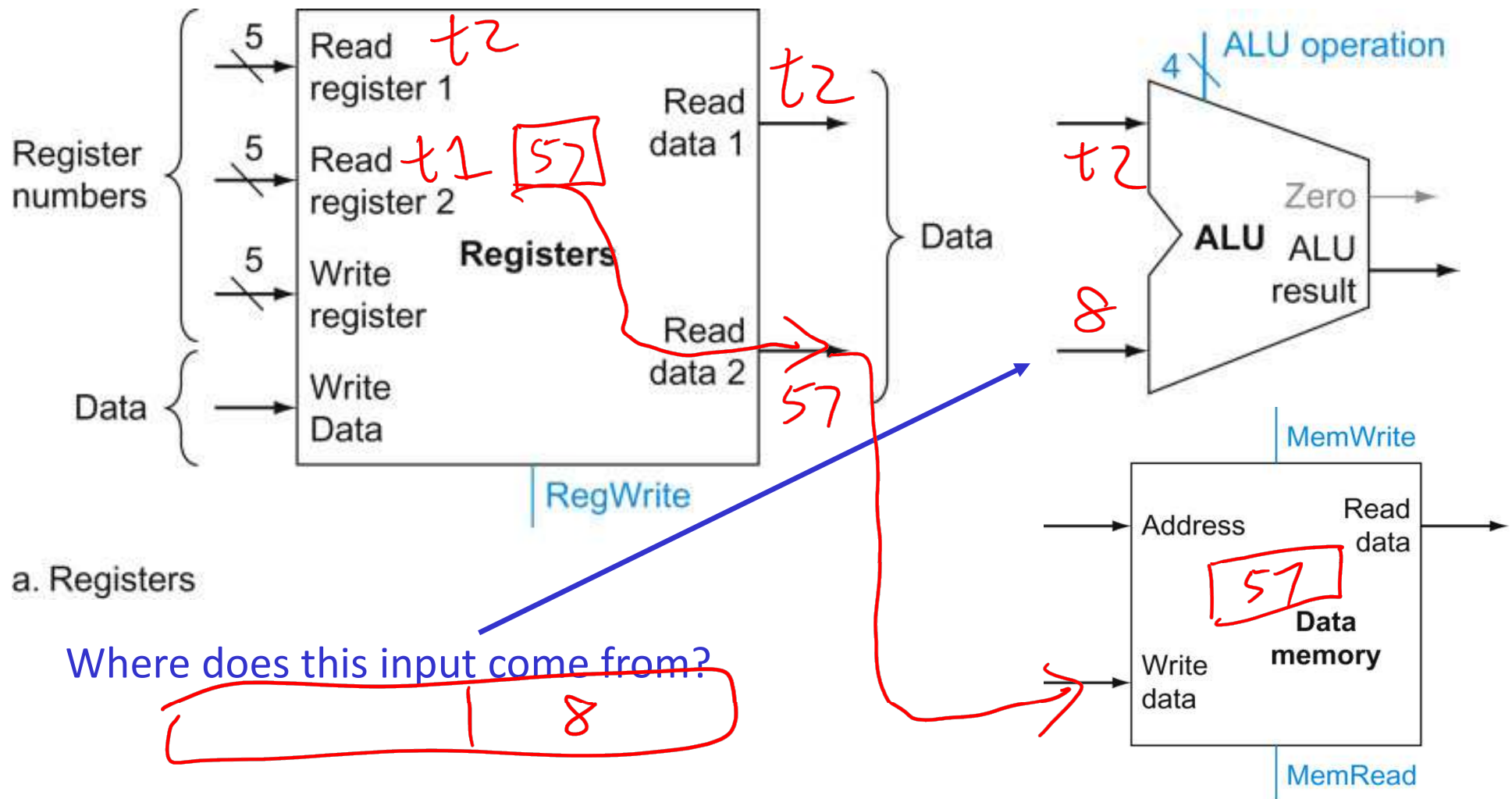- Instructions of the form `lw $t1, 8($t2)` and `sw $t1, 8($t2)`




Implementing J-type Instructions

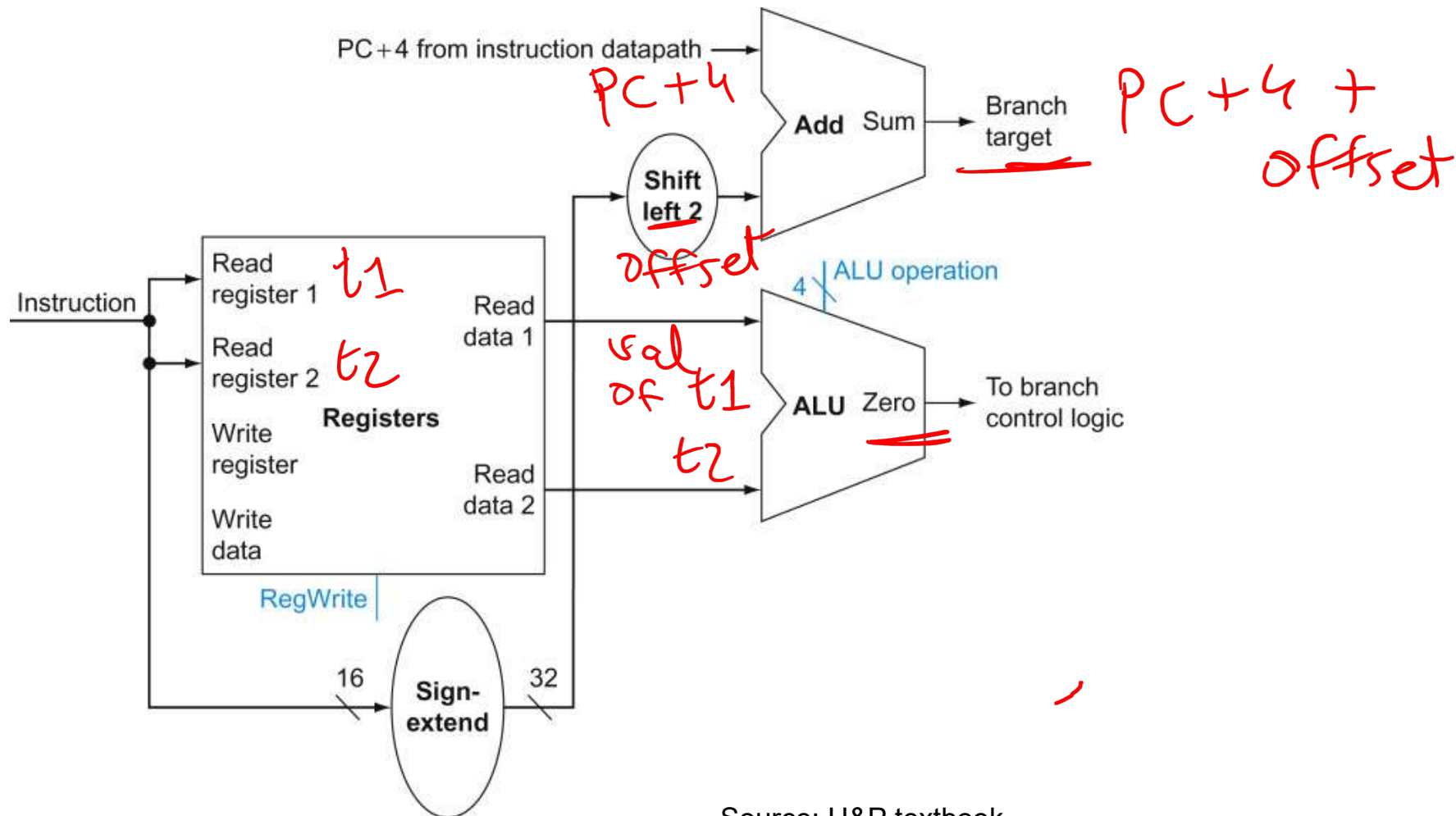- Instructions of the form beq \$t1, \$t2, offset




Source: H&P textbook


View from 10,000 Feet

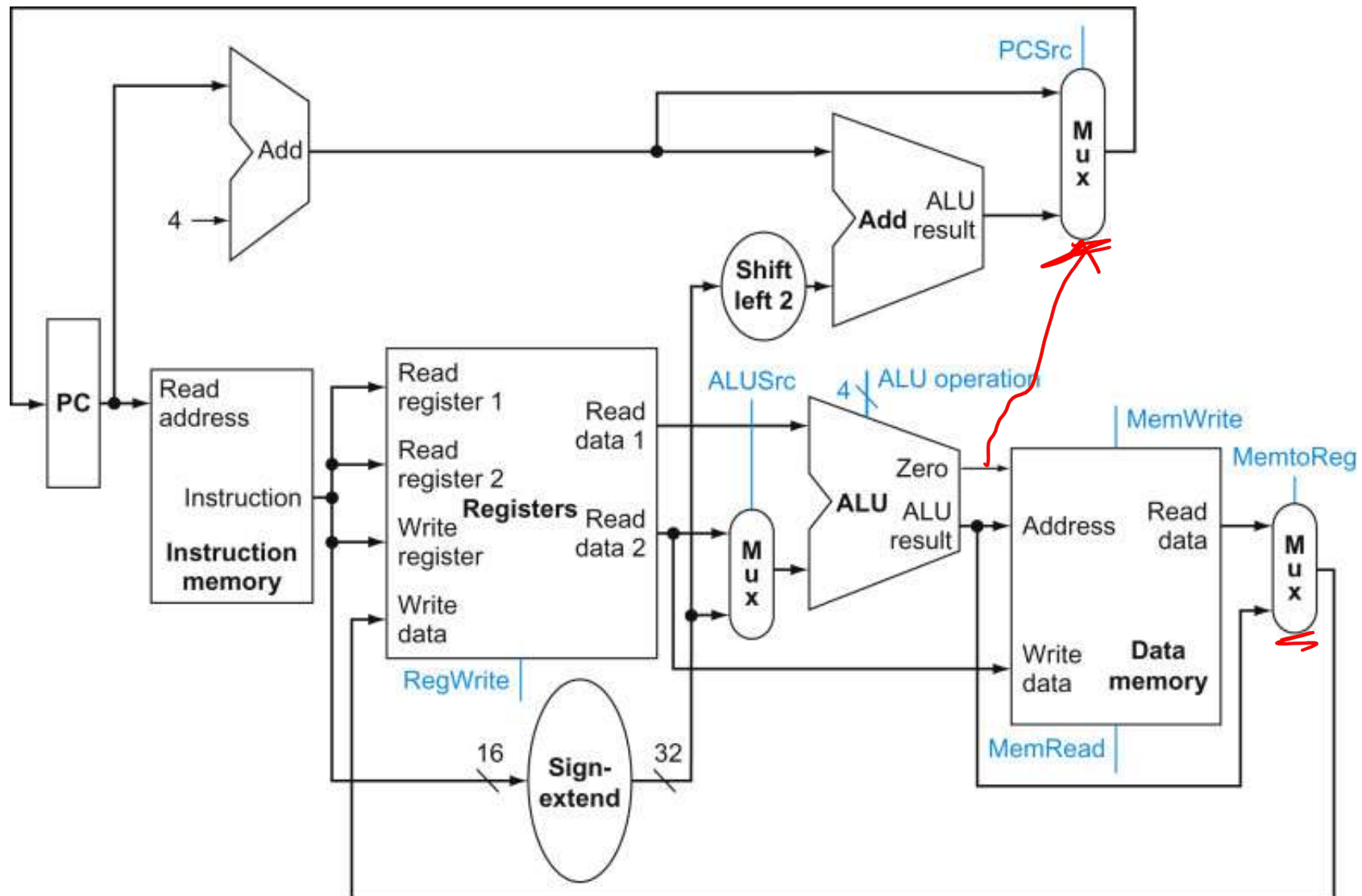

View from 5,000 Feet

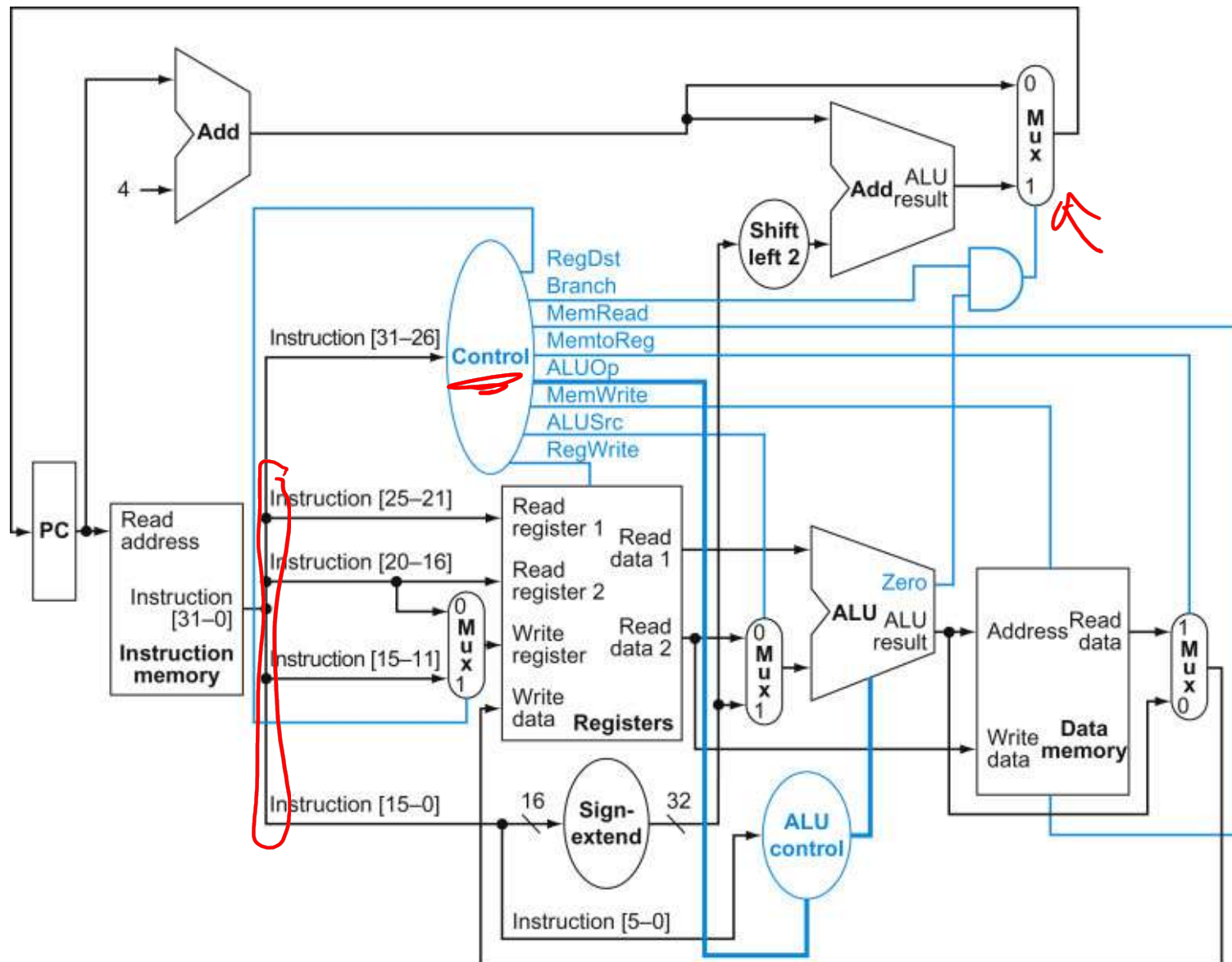

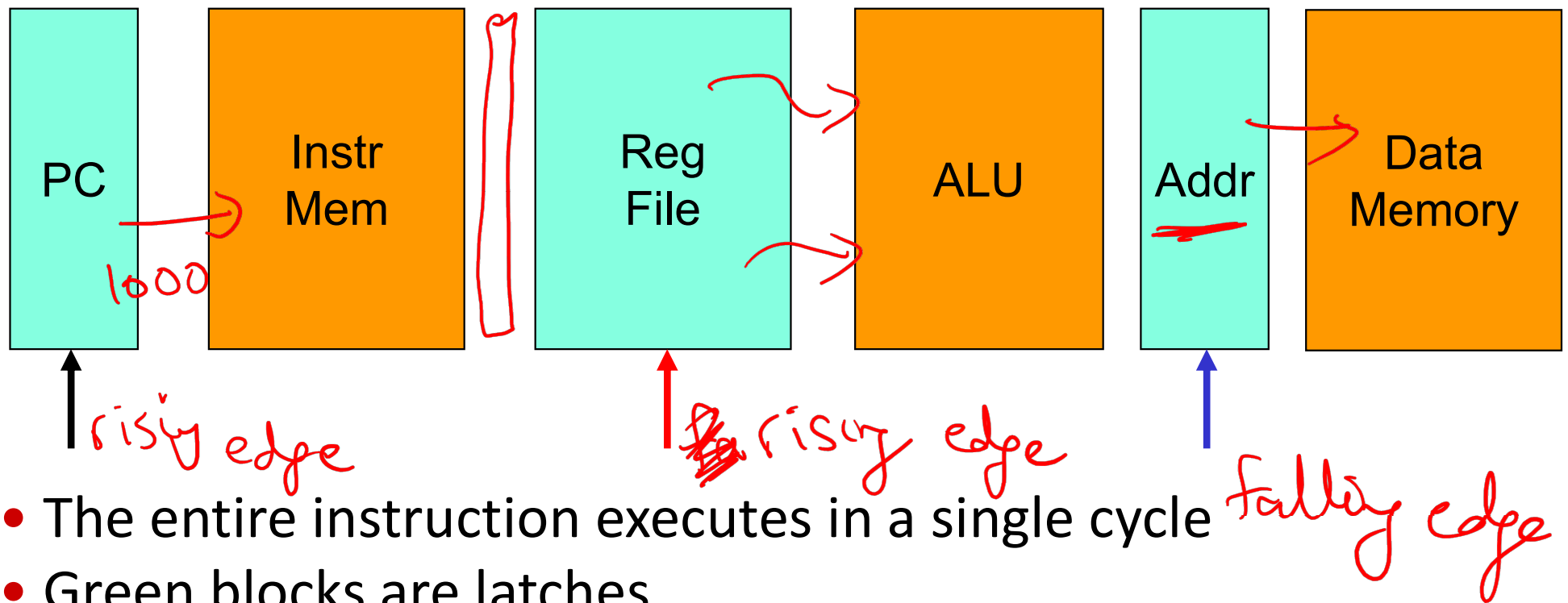Latches and Clocks in a Single-Cycle Design



- The entire instruction executes in a single cycle
- Green blocks are latches
- At the rising edge, a new PC is recorded
- At the rising edge, the result of the previous cycle is recorded
- At the falling edge, the address of LW/SW is recorded so we can access the data memory in the 2nd half of the cycle